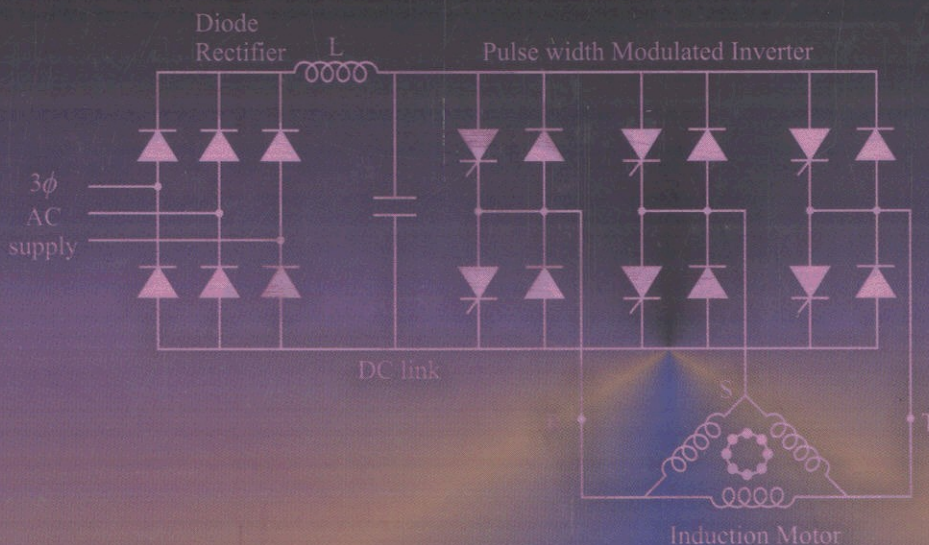


# Power Semiconductor Drives



S. Sivanagaraju  
M. Balasubba Reddy  
A. Mallikarjuna Prasad

# Contents

*Preface*

*ix*

*Acknowledgements*

*xi*

## **1. Control of DC Motor by Single-phase Converters 1-76**

- 1.1 Introduction 1
  - 1.1.1 Disadvantages of dc Motors 2
  - 1.1.2 Working Principle of dc Motor 2
- 1.2 Classification of dc Motors and Their Speed Control 3
  - 1.2.1 DC Shunt Motor or Separately Excited Motor 3
  - 1.2.2 DC Series Motor 5
  - 1.2.3 Compound Motor 6
- 1.3 Speed Control of dc Motors 7
  - 1.3.1 Flux Control Method 7
  - 1.3.2 Armature Voltage Control 8
  - 1.3.3 Voltage Control Methods 8
- 1.4 Block Diagram of Electrical Drive 10
  - 1.4.1 Parts of Electrical Drive 10
- 1.5 Single-phase Controlled Converter for Separately Excited dc Motor Drives 12
  - 1.5.1 Single-phase Semi-controlled Converter of dc Separately Excited Motor 12
  - 1.5.2 Single-phase Fully Controlled Converter of Separately Excited dc Motor 32
- 1.6 DC Series Motor Drives 55
  - 1.6.1 Single-phase Semi-controlled Converter of dc Series Excited Motor 56
  - 1.6.2 Single-phase Fully Controlled Converter dc Series Excited Motor 63

*Review Questions* 69

## **2. Control of DC Motor by Three-phase Converters 77-106**

- 2.1 Introduction 77
- 2.2 Three-phase Semi-converter Fed with Separately Excited dc Motor 77
  - 2.2.1 Continuous and Discontinuous Conduction 78
  - 2.2.2 Speed-Torque Characteristics 80

- 2.3 Three-phase Full-converter Fed with Separately Excited dc Motor 81
  - 2.3.1 Continuous Operation 81
  - 2.3.2 Speed-Torque Characteristics 83
- 2.4 Three-phase Semi-converter Fed dc Series Motor 95
  - 2.4.1 Continuous and Discontinuous Conduction 95
  - 2.4.2 Speed-Torque Characteristics 98
- 2.5 Three-phase Full-converter Fed dc Series Motor 100
  - 2.5.1 Speed-Torque Characteristics 102
- Review Questions 103*

### **3. Four-quadrant Operations of DC Drives 107-129**

- 3.1 Introduction to Four-quadrant Operations 107
- 3.2 Dual Converter for Multi-quadrant or Four-quadrant Operation 108
  - 3.2.1 Principle of Ideal Dual Converter 109
  - 3.2.2 Dual Converter without Circulating Current 110
  - 3.2.3 Dual Converter with Circulating Current 111
  - 3.2.4 Comparison of Circulating and Non-circulating Modes 111
  - 3.2.5 Single-phase Dual Converters 112
  - 3.2.6 Three-phase Dual Converters 113
- 3.3 Braking 118
  - 3.3.1 Mechanical or Friction Braking 119
  - 3.3.2 Electrical Braking 119
  - 3.3.3 Electrical Braking of dc Motors 120
- Review Questions 124*

### **4. Chopper Controlled DC Drives 130-205**

- 4.1 Introduction 130
  - 4.1.1 Resistance Control 130
  - 4.1.2 Motor Generator Set 130
  - 4.1.3 AC Link Chopper 130
- 4.2 Principle of Chopper Operation 131
- 4.3 Control Techniques Used in dc Choppers 132
  - 4.3.1 Time Ratio Control (TRC) 132
  - 4.3.2 Current Limit Control (CLC) 132
- 4.4 Chopper Configuration 132
- 4.5 Classification of Chopper Circuits 133
  - 4.5.1 First-quadrant Type Chopper 133
  - 4.5.2 Second-quadrant Type Chopper 140
  - 4.5.3 Four-quadrant Type Chopper 140
- 4.6 Chopper Control Performance Fed with Separately Excited dc Motors 141
  - 4.6.1 Motoring Control 141
  - 4.6.2 Regenerative Braking Control 154
  - 4.6.3 Motoring and Regenerating Control 156
  - 4.6.4 Dynamic Braking Control 157
  - 4.6.5 Regenerative Braking Control 182
  - 4.6.6 Motoring and Regenerating Control 184
  - 4.6.7 Dynamic Braking Control 185

- 4.7 Closed Loop Control of Drives 197
  - 4.7.1 Current Limit Control 198
  - 4.7.2 Closed Loop Torque Control 198
  - 4.7.3 Closed Loop Speed Control 199
  - 4.7.4 Closed Loop Control for dc Excited Motors 199

*Review Questions 201*

## **5. Stator Voltage Control of Induction Motor Drives 206–251**

- 5.1 Introduction 206
  - 5.1.1 Advantages of Squirrel Cage Induction Motors 207
- 5.2 Induction Motor Drives 208
  - 5.2.1 Steady State Analysis of Induction Motor at Constant Frequency 210
  - 5.2.2 Torque–Speed Characteristics of a Polyphase Induction Motor 216
- 5.3 Stator Voltage Control 230
  - 5.3.1 AC Voltage Controller for 3- $\phi$  Induction Motor 231
  - 5.3.2 Closed-loop Speed Control of Induction Motor using Stator Voltage Control 233
  - 5.3.3 Four-quadrant ac Voltage Controllers 233

*Review Questions 246*

## **6. Control of Induction Motor Drives through Rotor Frequency 252–282**

- 6.1 Introduction 252
- 6.2 Variable Frequency Characteristics 252
- 6.3 Block Diagram of Variable Frequency Speed Control 254
- 6.4 Voltage Source Inverter (VSI) Control 261
  - 6.4.1 Voltage Source Inverter Fed Induction Motor Drive 261
  - 6.4.2 Braking and Multi-quadrant Operation of VSI Induction Motor Drives 265
- 6.5 Variable Frequency Control from a Current Source 269
  - 6.5.1 Current Source Inverter 270
  - 6.5.2 Regenerative Braking and Multi-quadrant Operation 272
  - 6.5.3 Closed-loop Speed Control of CSI Drives 272
- 6.6 Comparison of VSI and CSI Drives 273
- 6.7 Cycloconverter Fed Induction Motor Drive 274
  - 6.7.1 Merits 275
  - 6.7.2 Demerits 275
- 6.8 Closed-loop Speed Control and Converter Rating for VSI as well as Cycloconverter Induction Motor Drives 275
  - 6.8.1 Operation 275
- 6.9 Pulse Width Modulated Inverter Fed Induction Motor Drive 276

*Review Questions 278*

## **7. Control of Induction Motor Drives from Rotor Side 283–327**

- 7.1 Introduction 283
- 7.2 Conventional Rotor Resistance Control 284
  - 7.2.1 Advantages 286
  - 7.2.2 Disadvantages 286

- 7.3 Static Rotor Resistance Control 291
  - 7.3.1 Performance and Its Analysis 293
- 7.4 Slip Power Recovery Schemes 303
  - 7.4.1 Static Scherbius Drive System 304
  - 7.4.2 Static Scherbius Drives 304
  - 7.4.3 Super-synchronous Speed Control 308
  - 7.4.4 Close-loop Control of Static Scherbius Drive 310
  - 7.4.5 Conventional Kramer System 315
  - 7.4.6 Static Kramer Drive 316
  - 7.4.7 Modified Static Kramer's Drive System 317

*Review Questions* 321

## **8. Control of Synchronous Motor Drives**

**328–359**

- 8.1 *Introduction* 328
- 8.2 Synchronous Motors 328
  - 8.2.1 Wound Field Synchronous Motor 328
  - 8.2.2 Cylindrical Rotor Wound Field Motor 330
  - 8.2.3 Salient Pole Wound Field Motor 332
  - 8.2.4 Permanent Magnet Motor 333
  - 8.2.5 Synchronous Reluctance Motor 334
  - 8.2.6 Damper Winding 334
- 8.3 Synchronous Operation from Fixed Frequency Supply 338
  - 8.3.1 Starting Torque 338
  - 8.3.2 Running Torque 339
  - 8.3.3 Pull-in Torque 339
  - 8.3.4 Pull-out Torque 339
  - 8.3.5 Braking 339
- 8.4 Speed Control of Synchronous Machines 343
  - 8.4.1 Separate Control of Synchronous Motors or True Synchronous Mode 343
  - 8.4.2 Closed Loop Self-control of Synchronous Motors 344
- 8.5 Load-commutated Inverter-fed Synchronous Motor Drive 346
- 8.6 Closed-loop Speed Control LCI Synchronous Motor Drive 348
  - 8.6.1 Advantages 349
- 8.7 Voltage Source Inverter Fed Synchronous Motor Drive 352
- 8.8 Cycloconverter Fed Synchronous Motor Drive 355
- 8.9 Features of Cycloconverter Fed Synchronous Motor Drives 356
  - 8.9.1 Line-commutated Cycloconverter 356
  - 8.9.2 Load-commutated Cycloconverter Fed Synchronous Motor 356

*Review Questions* 357