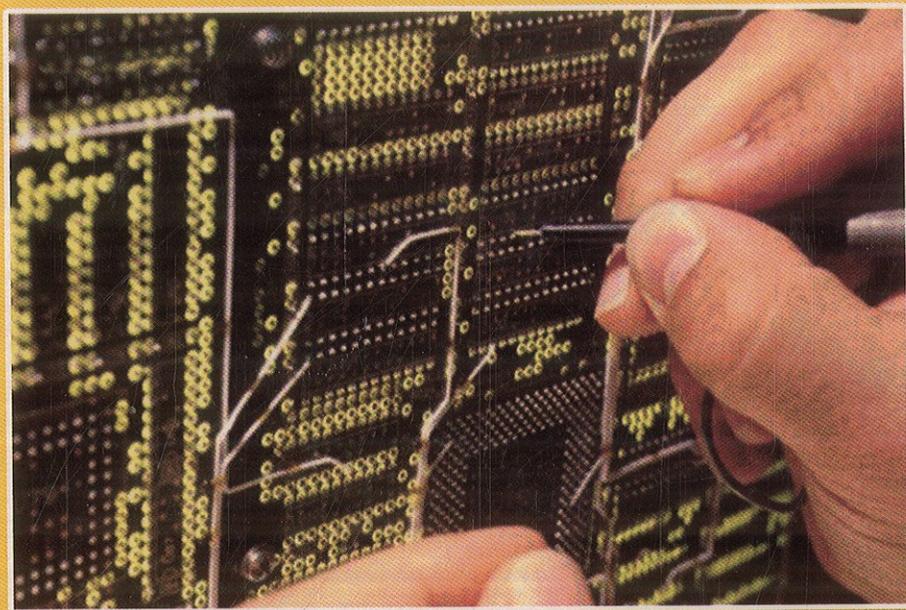


Electronics Engineering



O.N. Pandey

 **CRC Press**
Taylor & Francis Group

Contents

Preface

vii

1. BASICS OF ELECTRONICS	1–20
1.1 Introduction	1
1.2 Electronic Charge and Current	2
1.3 Electronic Circuit Components	2
1.4 Voltage and Current Relationships	5
1.5 Work, Power and Energy	6
1.6 SI Units	7
1.7 Voltage and Current Sources	8
1.8 Semiconductor Materials	9
1.9 <i>P-N</i> Junction and Depletion Layer	15
<i>Summary</i>	17
<i>Exercises</i>	19
2. SEMICONDUCTOR DIODES	21–68
2.1 Semiconductor Diode	21
2.2 <i>V-I</i> Characteristics	22
2.3 Ge, Si and GaAs Characteristics	24
2.4 Ideal and Practical <i>V-I</i> Characteristics	24
2.5 Diode Resistance	25

2.6	Diode Ratings	29
2.7	<i>P-N</i> Junction (Diode) as Rectifiers	30
2.8	Ripples Efficiency and Regulation	37
2.9	Efficiency of Full-wave Rectifier	38
2.10	Filters for Rectifiers	39
2.11	Clipping Circuits	44
2.12	Clamping Circuits	47
2.13	Voltage Multipliers	48
2.14	Zener Diodes	50
2.15	Temperature Coefficient	54
2.16	Zener Diode Application as Shunt Regulator	55
2.17	Diodes for Optoelectronics	56
2.18	Other Types of Diodes	58
	<i>Summary</i>	62
	<i>Exercises</i>	65
3.	BIPOLAR JUNCTION TRANSISTOR (BJT)	69–146
3.1	Basic Construction	69
3.2	Transistor Action	70
3.3	Circuit Configurations	72
3.4	Input/Output Characteristics	74
3.5	Mathematical Relationships	78
3.6	Biasing of Transistors	79
3.7	Graphical Analysis of CE Amplifier	87
3.8	Parameter Model	90
3.9	Hybrid Equivalent Circuit for Common Base (CB)	95
3.10	Hybrid Equivalent Circuit for Common Collector (CC)	95

3.11 Overall Current Gain	96
3.12 Overall Voltage Gain	97
<i>Summary</i>	142
<i>Exercises</i>	144

4. FIELD EFFECT TRANSISTOR (FET) 147–186

4.1 Introduction	147
4.2 Junction Field Effect Transistor (JFET)	148
4.3 Working Principle of JFET	149
4.4 Concept of Pinch-Off and Maximum Drain Saturation Current	151
4.5 Input and Transfer Characteristics	152
4.6 Parameters of JFET	153
4.7 JFET Biasing	154
4.8 JFET Connections	156
4.9 Metal Oxide Semiconductor Field Effect Transistor (MOSFET)	164
4.10 MOSFET Operation	166
4.11 Characteristics of MOSFET	168
<i>Summary</i>	182
<i>Exercises</i>	184

5. OPERATIONAL AMPLIFIER (OP-AMP) 187–220

5.1 Introduction	187
5.2 Op-amp Integrated Circuit	187
5.3 Op-amp Symbol	188
5.4 Concept of Ideal Op-amp	189
5.5 Inverting Amplifier	189
5.6 Non-inverting Amplifier	190

5.7	Unity Gain or Voltage Follower Amplifier	191
5.8	Op-amp as Adder or Summer	192
5.9	Op-amp as Difference Amplifier	193
5.10	Subtractor	195
5.11	Differentiator	195
5.12	Integrator	196
5.13	Op-amp Parameters	197
	<i>Summary</i>	217
	<i>Exercises</i>	218
6.	SWITCHING THEORY AND LOGIC DESIGN (STLD)	221–268
6.1	Introduction	221
6.2	Number System	221
6.3	Conversion of Bases	224
6.4	Binary Coded Decimal (BCD) Numbers	227
6.5	Binary Addition	227
6.6	Binary Subtraction	227
6.7	Boolean Algebra	227
6.8	Boolean Algebra Theorems Table	229
6.9	Logic Gates and Universal Gates	229
6.10	Canonical Forms	231
6.11	K-map	232
6.12	Simplification of Boolean Expression using K-map	233
6.13	Simplification in Sum of Product (SOP) form	234
	<i>Summary</i>	263
	<i>Exercises</i>	265

7. ELECTRONICS INSTRUMENTS	269–278
7.1 Digital Voltmeters (DVMs)	269
7.2 Digital Multimeters (DMMs)	272
7.3 Cathode Ray Oscilloscope (CRO)	273
7.4 Measurements Using CRO	275
<i>Summary</i>	276
<i>Exercises</i>	277
<i>Appendix</i>	279
<i>Glossary</i>	307
<i>Index</i>	323