# CONTENTS

|           | Preface to the SI Edition xii Preface xiii List of Symbols, Units, and Notation xix                                                                                                                                                                                                                                                                                                                   |  |  |  |  |
|-----------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|--|--|--|--|
| CHAPTER I | Introduction I                                                                                                                                                                                                                                                                                                                                                                                        |  |  |  |  |
|           | <ul> <li>Case Study: The Future Beckons: Will the Electric Power Industry Heed the Call? 2</li> <li>1.1 History of Electric Power Systems 10</li> <li>1.2 Present and Future Trends 17</li> <li>1.3 Electric Utility Industry Structure 21</li> <li>1.4 Computers in Power System Engineering 22</li> <li>1.5 PowerWorld Simulator 24</li> </ul>                                                      |  |  |  |  |
| CHAPTER 2 | Fundamentals 31                                                                                                                                                                                                                                                                                                                                                                                       |  |  |  |  |
|           | <ul> <li>Case Study: Making Microgrids Work 32</li> <li>2.1 Phasors 46</li> <li>2.2 Instantaneous Power in Single-Phase AC Circuits 47</li> <li>2.3 Complex Power 53</li> <li>2.4 Network Equations 58</li> <li>2.5 Balanced Three-Phase Circuits 60</li> <li>2.6 Power in Balanced Three-Phase Circuits 68</li> <li>2.7 Advantages of Balanced Three-Phase Versus Single-Phase Systems 74</li> </ul> |  |  |  |  |

### **CHAPTER 3** Power Transformers 90

| Case Study: PJM Manages Aging Transformer Fleet 91            |  |  |  |  |
|---------------------------------------------------------------|--|--|--|--|
| <b>3.1</b> The Ideal Transformer 96                           |  |  |  |  |
| <b>3.2</b> Equivalent Circuits for Practical Transformers 102 |  |  |  |  |
| 3.3 The Per-Unit System 108                                   |  |  |  |  |
| 3.4 Three-Phase Transformer Connections and Phase Shift       |  |  |  |  |
| 3.5 Per-Unit Equivalent Circuits of Balanced Three-Phase      |  |  |  |  |
| Two-Winding Transformers 121                                  |  |  |  |  |
| <b>3.6</b> Three-Winding Transformers 126                     |  |  |  |  |
| 3.7 Autotransformers 130                                      |  |  |  |  |

**3.8** Transformers with Off-Nominal Turns Ratios 131

| CHARTER | 4 | Transmission | 1:   | Dawa ma a taus | LEO |
|---------|---|--------------|------|----------------|-----|
| CHAPIEK | 4 | iransmission | Line | Parameters     | 159 |

| Case Study: Transmission Line Conductor Design Comes of Age      | 160 |
|------------------------------------------------------------------|-----|
| Case Study: Six Utilities Share Their Perspectives on Insulators | 164 |

- **4.1** Transmission Line Design Considerations 169
- **4.2** Resistance 174
- **4.3** Conductance 177
- **4.4** Inductance: Solid Cylindrical Conductor 178
- **4.5** Inductance: Single-Phase Two-Wire Line and Three-Phase Three-Wire Line with Equal Phase Spacing 183
- **4.6** Inductance: Composite Conductors, Unequal Phase Spacing, Bundled Conductors 185
- **4.7** Series Impedances: Three-Phase Line with Neutral Conductors and Earth Return 193
- **4.8** Electric Field and Voltage: Solid Cylindrical Conductor 199
- **4.9** Capacitance: Single-Phase Two-Wire Line and Three-Phase Three-Wire Line with Equal Phase Spacing 201
- **4.10** Capacitance: Stranded Conductors, Unequal Phase Spacing, Bundled Conductors 204
- **4.11** Shunt Admittances: Lines with Neutral Conductors and Earth Return 207
- **4.12** Electric Field Strength at Conductor Surfaces and at Ground Level 212
- **4.13** Parallel Circuit Three-Phase Lines 215

## CHAPTER 5 Transmission Lines: Steady-State Operation 233

Case Study: The ABCs of HVDC Transmission Technologies 234

- **5.1** Medium and Short Line Approximations 248
- **5.2** Transmission-Line Differential Equations 254
- 5.3 Equivalent  $\pi$  Circuit 260
- **5.4** Lossless Lines 262
- **5.5** Maximum Power Flow 271
- **5.6** Line Loadability 273
- **5.7** Reactive Compensation Techniques 277

#### **CHAPTER 6 Power Flows 294**

Case Study: Future Vision 295

Case Study: Characteristics of Wind Turbine Generators for Wind Power Plants 305

- 6.1 Direct Solutions to Linear Algebraic Equations:
  - Gauss Elimination 311
- **6.2** Iterative Solutions to Linear Algebraic Equations: Jacobi and Gauss–Seidel 315
- **6.3** Iterative Solutions to Nonlinear Algebraic Equations: Newton–Raphson 321

|           | <ul> <li>6.4 The Power-Flow Problem 325</li> <li>6.5 Power-Flow Solution by Gauss-Seidel 331</li> <li>6.6 Power-Flow Solution by Newton-Raphson 334</li> <li>6.7 Control of Power Flow 343</li> <li>6.8 Sparsity Techniques 349</li> <li>6.9 Fast Decoupled Power Flow 352</li> <li>6.10 The "DC" Power Flow 353</li> <li>6.11 Power-Flow Modeling of Wind Generation 354</li> <li>Design Projects 1-5 366</li> </ul>                                                                                                                                                      |
|-----------|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| CHAPTER 7 | Symmetrical Faults 379                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                     |
|           | <ul> <li>Case Study: The Problem of Arcing Faults in Low-Voltage Power Distribution Systems 380</li> <li>7.1 Series R-L Circuit Transients 382</li> <li>7.2 Three-Phase Short Circuit—Unloaded Synchronous Machine 385</li> <li>7.3 Power System Three-Phase Short Circuits 389</li> <li>7.4 Bus Impedance Matrix 392</li> <li>7.5 Circuit Breaker and Fuse Selection 400</li> <li>Design Project 4 (continued) 417</li> </ul>                                                                                                                                             |
| CHAPTER 8 | Symmetrical Components 419                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                 |
|           | <ul> <li>Case Study: Circuit Breakers Go High Voltage 421</li> <li>8.1 Definition of Symmetrical Components 428</li> <li>8.2 Sequence Networks of Impedance Loads 433</li> <li>8.3 Sequence Networks of Series Impedances 441</li> <li>8.4 Sequence Networks of Three-Phase Lines 443</li> <li>8.5 Sequence Networks of Rotating Machines 445</li> <li>8.6 Per-Unit Sequence Models of Three-Phase Two-Winding Transformers 451</li> <li>8.7 Per-Unit Sequence Models of Three-Phase Three-Winding Transformers 456</li> <li>8.8 Power in Sequence Networks 459</li> </ul> |
| CHAPTER 9 | Unsymmetrical Faults 471                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                   |
|           | Case Study: Fires at U.S. Utilities 472  9.1 System Representation 473  9.2 Single Line-to-Ground Fault 478  9.3 Line-to-Line Fault 483  9.4 Double Line-to-Ground Fault 485  9.5 Sequence Bus Impedance Matrices 492  Design Project 4 (continued) 512  Design Project 6 513                                                                                                                                                                                                                                                                                              |

### **CHAPTER 10** System Protection 516

| Casa | Ctudo  | The  | Future | of | Dower | Trar   | smission   | 519   | Q |
|------|--------|------|--------|----|-------|--------|------------|-------|---|
| Case | Stuav: | i ne | ruure  | OL | Power | T Tall | ISHHISSIOH | - 216 | O |

- **10.1** System Protection Components 525
- **10.2** Instrument Transformers 526
- 10.3 Overcurrent Relays 533
- **10.4** Radial System Protection 537
- 10.5 Reclosers and Fuses 541
- 10.6 Directional Relays 545
- 10.7 Protection of Two-Source System with Directional Relays 546
- **10.8** Zones of Protection 547
- 10.9 Line Protection with Impedance (Distance) Relays 551
- 10.10 Differential Relays 557
- **10.11** Bus Protection with Differential Relays 559
- 10.12 Transformer Protection with Differential Relays 560
- 10.13 Pilot Relaying 565
- 10.14 Digital Relaying 566

### **CHAPTER II Transient Stability 579**

Case Study: Real-Time Dynamic Security Assessment 581

- 11.1 The Swing Equation 590
- 11.2 Simplified Synchronous Machine Model and System Equivalents 596
- 11.3 The Equal-Area Criterion 598
- 11.4 Numerical Integration of the Swing Equation 608
- 11.5 Multimachine Stability 613
- 11.6 A Two-Axis Synchronous Machine Model 621
- 11.7 Wind Turbine Machine Models 625
- 11.8 Design Methods for Improving Transient Stability 632

### **CHAPTER 12 Power System Controls 639**

Case Study: Overcoming Restoration Challenges Associated with Major Power System Disturbances 642

- **12.1** Generator-Voltage Control 652
- **12.2** Turbine-Governor Control 657
- **12.3** Load-Frequency Control 663
- 12.4 Economic Dispatch 667
- 12.5 Optimal Power Flow 680

## CHAPTER 13 Transmission Lines: Transient Operation 690

Case Study: VariSTAR® Type AZE Surge Arresters 691

Case Study: Change in the Air 695

- 13.1 Traveling Waves on Single-Phase Lossless Lines 707
- **13.2** Boundary Conditions for Single-Phase Lossless Lines 710

#### CONTENTS

- 13.3 Bewley Lattice Diagram 719
- 13.4 Discrete-Time Models of Single-Phase Lossless Lines and Lumped RLC Elements 724
- **13.5** Lossy Lines 731
- 13.6 Multiconductor Lines 735
- **13.7** Power System Overvoltages 738
- 13.8 Insulation Coordination 745

#### **CHAPTER 14 POWER DISTRIBUTION 757**

Case Study: The Path of the Smart Grid 759

- **14.1** Introduction to Distribution 770
- **14.2** Primary Distribution 772
- 14.3 Secondary Distribution 780
- **14.4** Transformers in Distribution Systems 785
- 14.5 Shunt Capacitors in Distribution Systems 795
- **14.6** Distribution Software 800
- 14.7 Distribution Reliability 801
- 14.8 Distribution Automation 804
- **14.9** Smart Grids 807

Appendix 814 Index 818