

Hussein Baher

SIGNAL PROCESSING AND INTEGRATED CIRCUITS

 WILEY



Contents

About the Author	xv
-------------------------	-----------

Preface	xvii
----------------	-------------

Part I PERSPECTIVE

1	Analog, Digital and Mixed-mode Signal Processing	3
1.1	Digital Signal Processing	3
1.2	Moore's Law and the "Cleverness" Factor	3
1.3	System on a Chip	3
1.4	Analog and Mixed-mode Signal Processing	4
1.5	Scope	5

Part II ANALOG (CONTINUOUS-TIME) AND DIGITAL SIGNAL PROCESSING

2	Analog Continuous-time Signals and Systems	9
2.1	Introduction	9
2.2	The Fourier Series in Signal Analysis and Function Approximation	9
2.2.1	<i>Definitions</i>	9
2.2.2	<i>The Time and Discrete Frequency Domains</i>	10
2.2.3	<i>Convolution</i>	12
2.2.4	<i>Parseval's Theorem and Power Spectrum</i>	12
2.2.5	<i>The Gibbs' Phenomenon</i>	12
2.2.6	<i>Window Functions</i>	13
2.3	The Fourier Transformation and Generalized Signals	14
2.3.1	<i>Definitions and Properties</i>	14
2.3.2	<i>Parseval's Theorem and Energy Spectra</i>	16
2.3.3	<i>Correlation Functions</i>	17
2.3.4	<i>The Unit Impulse and Generalized Signals</i>	17
2.3.5	<i>The Impulse Response and System Function</i>	18
2.3.6	<i>Periodic Signals</i>	19
2.3.7	<i>The Uncertainty Principle</i>	19
2.4	The Laplace Transform and Analog Systems	19
2.4.1	<i>The Complex Frequency</i>	19

2.4.2	<i>Properties of the Laplace Transform</i>	21
2.4.3	<i>The System Function</i>	22
2.5	Elementary Signal Processing Building Blocks	24
2.5.1	<i>Realization of the Elementary Building Blocks using Operational Amplifier Circuits</i>	24
2.6	Realization of Analog System Functions	29
2.6.1	<i>General Principles and the Use of Op Amp Circuits</i>	29
2.6.2	<i>Realization Using OTAs and $G_m - C$ Circuits</i>	32
2.7	Conclusion	34
	Problems	34
3	Design of Analog Filters	39
3.1	Introduction	39
3.2	Ideal Filters	39
3.3	Amplitude-oriented Design	43
3.3.1	<i>Maximally Flat Response in both Pass-band and Stop-band</i>	44
3.3.2	<i>Chebyshev Response</i>	46
3.3.3	<i>Elliptic Function Response</i>	48
3.4	Frequency Transformations	49
3.4.1	<i>Low-pass to Low-pass Transformation</i>	50
3.4.2	<i>Low-pass to High-pass Transformation</i>	50
3.4.3	<i>Low-pass to Band-pass Transformation</i>	50
3.4.4	<i>Low-pass to Band-stop Transformation</i>	51
3.5	Examples	52
3.6	Phase-oriented Design	54
3.6.1	<i>Phase and Delay Functions</i>	54
3.6.2	<i>Maximally Flat Delay Response</i>	56
3.7	Passive Filters	58
3.8	Active Filters	59
3.9	Use of MATLAB® for the Design of Analog Filters	62
3.9.1	<i>Butterworth Filters</i>	62
3.9.2	<i>Chebyshev Filters</i>	63
3.9.3	<i>Elliptic Filters</i>	63
3.9.4	<i>Bessel Filters</i>	64
3.10	Examples of the use of MATLAB®	65
3.11	A Comprehensive Application: Pulse Shaping for Data Transmission	67
3.12	Conclusion	70
	Problems	72
4	Discrete Signals and Systems	75
4.1	Introduction	75
4.2	Digitization of Analog Signals	75
4.2.1	<i>Sampling</i>	76
4.2.2	<i>Quantization and Encoding</i>	84
4.3	Discrete Signals and Systems	85
4.4	Digital Filters	87
4.5	Conclusion	92
	Problems	93

5	Design of Digital Filters	95
5.1	Introduction	95
5.2	General Considerations	95
5.3	Amplitude-oriented Design of IIR Filters	98
5.3.1	<i>Low-pass Filters</i>	98
5.3.2	<i>High-pass Filters</i>	105
5.3.3	<i>Band-pass Filters</i>	107
5.3.4	<i>Band-stop Filters</i>	108
5.4	Phase-oriented Design of IIR Filters	108
5.4.1	<i>General Considerations</i>	108
5.4.2	<i>Maximally Flat Group-delay Response</i>	109
5.5	FIR Filters	111
5.5.1	<i>The Exact Linear Phase Property</i>	111
5.5.2	<i>Fourier-coefficient Filter Design</i>	118
5.5.3	<i>Monotonic Amplitude Response with the Optimum Number of Constraints</i>	128
5.5.4	<i>Optimum Equiripple Response in both Passband and Stopband</i>	128
5.6	Comparison Between IIR and FIR Filters	133
5.7	Use of MATLAB® for the Design of Digital Filters	133
5.7.1	<i>Butterworth IIR Filters</i>	134
5.7.2	<i>Chebyshev IIR Filters</i>	136
5.7.3	<i>Elliptic IIR Filters</i>	138
5.7.4	<i>Realization of the Filter</i>	140
5.7.5	<i>Linear Phase FIR Filters</i>	140
5.8	A Comprehensive Application: Pulse Shaping for Data Transmission	142
5.8.1	<i>Optimal Design</i>	142
5.8.2	<i>Use of MATLAB® for the Design of Data Transmission Filters</i>	144
5.9	Conclusion	146
	Problems	146
6	The Fast Fourier Transform and its Applications	149
6.1	Introduction	149
6.2	Periodic Signals	150
6.3	Non-periodic Signals	153
6.4	The Discrete Fourier Transform	157
6.5	The Fast Fourier Transform Algorithms	160
6.5.1	<i>Decimation-in-time Fast Fourier Transform</i>	161
6.5.2	<i>Decimation-in-frequency Fast Fourier Transform</i>	166
6.5.3	<i>Radix 4 Fast Fourier Transform</i>	168
6.6	Properties of the Discrete Fourier Transform	170
6.6.1	<i>Linearity</i>	170
6.6.2	<i>Circular Convolution</i>	170
6.6.3	<i>Shifting</i>	171
6.6.4	<i>Symmetry and Conjugate Pairs</i>	172
6.6.5	<i>Parseval's Relation and Power Spectrum</i>	173
6.6.6	<i>Circular Correlation</i>	174
6.6.7	<i>Relation to the z-transform</i>	175
6.7	Spectral Analysis Using the FFT	176

6.7.1	<i>Evaluation of the Fourier Integral</i>	176
6.7.2	<i>Evaluation of the Fourier Coefficients</i>	178
6.8	Spectral Windows	180
6.8.1	<i>Continuous-time Signals</i>	180
6.8.2	<i>Discrete-time Signals</i>	184
6.9	Fast Convolution, Filtering and Correlation Using the FFT	184
6.9.1	<i>Circular (Periodic) Convolution</i>	184
6.9.2	<i>Non-periodic Convolution</i>	185
6.9.3	<i>Filtering and Sectioned Convolution</i>	185
6.9.4	<i>Fast Correlation</i>	188
6.10	Use of MATLAB®	190
6.11	Conclusion	190
	Problems	190
7	Stochastic Signals and Power Spectra	193
7.1	Introduction	193
7.2	Random Variables	193
7.2.1	<i>Probability Distribution Function</i>	193
7.2.2	<i>Probability Density Function</i>	194
7.2.3	<i>Joint Distributions</i>	195
7.2.4	<i>Statistical Parameters</i>	195
7.3	Analog Stochastic Processes	198
7.3.1	<i>Statistics of Stochastic Processes</i>	198
7.3.2	<i>Stationary Processes</i>	200
7.3.3	<i>Time Averages</i>	201
7.3.4	<i>Ergodicity</i>	201
7.3.5	<i>Power Spectra of Stochastic Signals</i>	203
7.3.6	<i>Signals through Linear Systems</i>	207
7.4	Discrete-time Stochastic Processes	209
7.4.1	<i>Statistical Parameters</i>	209
7.4.2	<i>Stationary Processes</i>	209
7.5	Power Spectrum Estimation	213
7.5.1	<i>Continuous-time Signals</i>	213
7.5.2	<i>Discrete-time Signals</i>	216
7.6	Conclusion	217
	Problems	217
8	Finite Word-length Effects in Digital Signal Processors	219
8.1	Introduction	219
8.2	Input Signal Quantization Errors	221
8.3	Coefficient Quantization Effects	225
8.4	Effect of Round-off Accumulation	227
8.4.1	<i>Round-off Accumulation without Coefficient Quantization</i>	228
8.4.2	<i>Round-off Accumulation with Coefficient Quantization</i>	235
8.5	Auto-oscillations: Overflow and Limit Cycles	238
8.5.1	<i>Overflow Oscillations</i>	238
8.5.2	<i>Limit Cycles and the Dead-band Effect</i>	241

8.6	Conclusion Problems	244
9	Linear Estimation, System Modelling and Adaptive Filters	245
9.1	Introduction	245
9.2	Mean-square Approximation	245
9.2.1	<i>Analog Signals</i>	245
9.2.2	<i>Discrete Signals</i>	247
9.3	Linear Estimation, Modelling and Optimum Filters	248
9.4	Optimum Minimum Mean-square Error Analog Estimation	250
9.4.1	<i>Smoothing by Non-causal Wiener Filters</i>	250
9.4.2	<i>Causal Wiener Filters</i>	253
9.5	The Matched Filter	253
9.6	Discrete-time Linear Estimation	255
9.6.1	<i>Non-recursive Wiener Filtering</i>	256
9.6.2	<i>Adaptive Filtering Using the Minimum Mean Square Error Gradient Algorithm</i>	260
9.6.3	<i>The Least Mean Square Error Gradient Algorithm</i>	263
9.7	Adaptive IIR Filtering and System Modelling	263
9.8	An Application of Adaptive Filters: Echo Cancellers for Satellite Transmission of Speech Signals	266
9.9	Conclusion	267

Part III ANALOG MOS INTEGRATED CIRCUITS FOR SIGNAL PROCESSING

10	MOS Transistor Operation and Integrated Circuit Fabrication	271
10.1	Introduction	271
10.2	The MOS Transistor	271
10.2.1	<i>Operation</i>	272
10.2.2	<i>The Transconductance</i>	276
10.2.3	<i>Channel Length Modulation</i>	278
10.2.4	<i>PMOS Transistors and CMOS Circuits</i>	279
10.2.5	<i>The Depletion-type MOSFET</i>	280
10.3	Integrated Circuit Fabrication	280
10.3.1	<i>Wafer Preparation</i>	281
10.3.2	<i>Diffusion and Ion Implantation</i>	281
10.3.3	<i>Oxidation</i>	283
10.3.4	<i>Photolithography</i>	285
10.3.5	<i>Chemical Vapour Deposition</i>	286
10.3.6	<i>Metallization</i>	287
10.3.7	<i>MOSFET Processing Steps</i>	287
10.4	Layout and Area Considerations for IC MOSFETs	288
10.5	Noise In MOSFETs	290
10.5.1	<i>Shot Noise</i>	290
10.5.2	<i>Thermal Noise</i>	290

10.5.3	<i>Flicker (1/f) Noise</i>	290
10.5.4	<i>Modelling of Noise</i>	290
	Problems	291
11	Basic Integrated Circuits Building Blocks	293
11.1	Introduction	293
11.2	MOS Active Resistors and Load Devices	293
11.3	MOS Amplifiers	295
11.3.1	<i>NMOS Amplifier with Enhancement Load</i>	295
11.3.2	<i>Effect of the Substrate</i>	296
11.3.3	<i>NMOS Amplifier with Depletion Load</i>	297
11.3.4	<i>The Source Follower</i>	298
11.4	High Frequency Considerations	300
11.4.1	<i>Parasitic Capacitances</i>	300
11.4.2	<i>The Cascode Amplifier</i>	303
11.5	The Current Mirror	304
11.6	The CMOS Amplifier	305
11.7	Conclusion	308
	Problems	308
12	Two-stage CMOS Operational Amplifiers	311
12.1	Introduction	311
12.2	Op Amp Performance Parameters	311
12.3	Feedback Amplifier Fundamentals	314
12.4	The CMOS Differential Amplifier	316
12.5	The Two-stage CMOS Op Amp	321
12.5.1	<i>The dc Voltage Gain</i>	322
12.5.2	<i>The Frequency Response</i>	322
12.5.3	<i>The Nulling Resistor</i>	323
12.5.4	<i>The Slew Rate and Settling Time</i>	325
12.5.5	<i>The Input Common-mode Range and CMRR</i>	325
12.5.6	<i>Summary of the Two-stage CMOS Op Amp Design Calculations</i>	327
12.6	A Complete Design Example	329
12.7	Practical Considerations and Other Non-ideal Effects in Operational Amplifier Design	332
12.7.1	<i>Power Supply Rejection</i>	332
12.7.2	<i>dc Offset Voltage</i>	332
12.7.3	<i>Noise Performance</i>	332
12.8	Conclusion	334
	Problems	334
13	High Performance CMOS Operational Amplifiers and Operational Transconductance Amplifiers	337
13.1	Introduction	337
13.2	Cascode CMOS Op Amps	337
13.3	The Folded Cascode Op Amp	338
13.4	Low-noise Operational Amplifiers	340
13.4.1	<i>Low-noise Design by Control of Device Geometries</i>	340

13.4.2	<i>Noise Reduction by Correlated Double Sampling</i>	342
13.4.3	<i>Chopper-stabilized Operational Amplifiers</i>	342
13.5	High-frequency Operational Amplifiers	344
13.5.1	<i>Settling Time Considerations</i>	345
13.6	Fully Differential Balanced Topology	346
13.7	Operational Transconductance Amplifiers	353
13.8	Conclusion	353
	Problems	354
14	Capacitors, Switches and the Occasional Passive Resistor	357
14.1	Introduction	357
14.2	MOS Capacitors	357
14.2.1	<i>Capacitor Structures</i>	357
14.2.2	<i>Parasitic Capacitances</i>	358
14.2.3	<i>Capacitor-ratio Errors</i>	358
14.3	The MOS Switch	362
14.3.1	<i>A Simple Switch</i>	362
14.3.2	<i>Clock Feed-through</i>	362
14.3.3	<i>The CMOS Switch: Transmission Gate</i>	364
14.4	MOS Passive Resistors	366
14.5	Conclusion	366

Part IV SWITCHED-CAPACITOR AND MIXED-MODE SIGNAL PROCESSING

15	Design of Microelectronic Switched-capacitor Filters	369
15.1	Introduction	369
15.2	Sampled and Held Signals	371
15.3	Amplitude-oriented Filters of the Lossless Discrete Integrator Type	374
15.3.1	<i>The State-variable Ladder Filter</i>	374
15.3.2	<i>Strays-insensitive LDI Ladders</i>	381
15.3.3	<i>An Approximate Design Technique</i>	384
15.4	Filters Derived from Passive Lumped Prototypes	388
15.5	Cascade Design	396
15.6	Applications in Telecommunications: Speech Codecs and Data Modems	399
15.6.1	<i>CODECs</i>	399
15.6.2	<i>Data Modems</i>	399
15.7	Conclusion	400
	Problems	400
16	Non-ideal Effects and Practical Considerations in Microelectronic Switched-capacitor Filters	403
16.1	Introduction	403
16.2	Effect of Finite Op Amp Gain	403
16.3	Effect of Finite Bandwidth and Slew Rate of Op Amps	405
16.4	Effect of Finite Op Amp Output Resistance	405
16.5	Scaling for Maximum Dynamic Range	405

16.6	Scaling for Minimum Capacitance	407
16.7	Fully Differential Balanced Designs	407
16.8	More on Parasitic Capacitances and Switch Noise	410
16.9	Pre-filtering and Post-filtering Requirements	412
16.10	Programmable Filters	413
16.11	Layout Considerations	415
16.12	Conclusion	416
17	Integrated Sigma-Delta Data Converters: Extension and Comprehensive Application of Analog and Digital Signal Processing	417
17.1	Motivation and General Considerations	417
17.2	The First-order Converter	419
17.3	The Second-order Converter	423
17.4	Decimation and Digital Filtering	426
	17.4.1 Principles	426
	17.4.2 Decimator Structures	429
17.5	Simulation and Performance Evaluation	433
17.6	A Case Study: Fourth-order Converter	435
17.7	Conclusion	438
	Answers to Selected Problems	439
	References	445
	Index	447