

Contents

	<i>List of contributors</i>	page xiv
	<i>Preface</i>	xv
1	Silicon LDMOS and VDMOS transistors: physics, design, and technology	1
	Wayne Burger and Christopher P. Dragon	
1.1	Technology overview	1
1.1.1	Introduction/history	1
1.2	LDMOS and VDMOS construction	2
1.2.1	LDMOS	2
1.2.2	VDMOS	8
1.3	Device physics	10
1.3.1	Current transport	10
1.3.2	Behavior of parasitic elements/models	12
1.3.3	BV_{DSS} , R_{DSon} , HCI boundaries	17
1.3.4	Snapback/ruggedness	22
1.3.5	Operating voltage considerations	26
1.4	Design/layout	27
1.4.1	Top-down finger layout	27
1.4.2	Bond pad manifolds	29
1.4.3	Metal design – electromigration	30
1.4.4	Thermal	32
1.4.5	Operating voltage considerations	34
1.4.6	Frequency considerations: gate length, gate width, resistors	36
1.4.7	HVICs	37
	References	39
2	GaAs FETs – physics, design, and models	42
	Rob Davis	
2.1	Introduction	42
2.1.1	Properties of GaAs and related compounds	43
2.1.2	The Schottky barrier gate and the MESFET	45
2.1.3	The Pf^2 limit	45
2.1.4	Types of GaAs FET	46

Contents

2.2	Power device physics	51
2.2.1	The device I – V characteristic and loadline	51
2.2.2	The dynamic I – V characteristic	53
2.2.3	The consequences of trapping effects	54
2.2.4	Device breakdown	57
2.2.5	Breakdown mechanisms and optimisation	58
2.2.6	Comments on GaAs FET breakdown ratings	59
2.2.7	The FET equivalent circuit	60
2.2.8	Device gain and figures of merit	61
2.3	Device design	63
2.3.1	Power device design	63
2.3.2	FET channel and recess design	63
2.3.3	Power cell design	67
2.3.4	Power cell combination	71
2.3.5	Thermal design	72
2.4	Device fabrication	74
2.4.1	Overview	74
2.4.2	Key process steps	75
2.4.3	Low-cost GaAs device fabrication	81
2.4.4	Packaging	81
2.5	Models	84
2.5.1	Device models	84
2.5.2	Small-signal models	84
2.5.3	Large signal models	85
2.5.4	Load-pull	89
2.6	Concluding remarks	90
	References	91

3 Wide band gap transistors – SiC and GaN – physics, design and models 103

Robert J. Trew

3.1	Introduction	103
3.2	Background	105
3.2.1	SiC transistors	106
3.2.2	AlGaN/GaN transistors	108
3.3	Material parameters	111
3.4	Transistor amplifier operating principles	115
3.5	Device design and RF performance	118
3.5.1	4H-SiC MESFET amplifier	120
3.5.2	AlGaN/GaN HFET amplifier	123
3.6	Transistor DC and large-signal RF models	125
3.6.1	Equivalent circuit transistor models	125
3.6.2	Physics-based large-signal transistor models	128

3.7	Large-signal effects	130
3.7.1	Space charge limited current transport	130
3.7.2	Nonlinear source and drain resistance	133
3.7.3	Gate leakage	144
3.7.4	Reliability and time-dependent performance degradation	146
3.8	Summary	152
	References	153
4	Amplifier classes, A–S	159
	Steve C. Cripps	
4.1	Introduction	159
4.2	Active device models	161
4.3	Class A	162
4.4	Class AB and Class B	164
4.5	Class C	171
4.6	Class F	173
4.7	Class J	176
4.8	Inverted modes, inverted Class F	179
4.9	Class E	181
4.10	Class S	183
4.11	Multimodes	184
4.12	Conclusions	186
	References	186
5	Computer-aided design of power amplifiers	188
	Stephen Maas	
5.1	Introduction	188
5.2	Methods of analysis	188
5.2.1	Linear analysis	188
5.2.2	Harmonic-balance analysis	193
5.2.3	Time-domain analysis	202
5.2.4	Applications of analytical methods	205
5.3	Passive circuit structures and simulation accuracy	205
5.3.1	Scattering parameter models	206
5.3.2	Closed-form models	208
5.3.3	Models from EM simulation	210
5.3.4	Database models	212
5.3.5	Parasitic extraction	212
5.4	Solid-state device models	213
5.4.1	Power device models	213
5.4.2	Modeling cell interconnections in large devices	213
5.4.3	Thermal effects in device models	214

Contents

5.5	Special aspects of power-amplifier modeling	216
5.5.1	Loss in circuit metalizations	217
5.5.2	Loss in circuit components	219
5.5.3	Bond wires	219
5.6	Practical aspects of nonlinear circuit simulation	221
5.6.1	Convergence difficulties	221
5.6.2	SPICE models in harmonic-balance analysis	226
5.6.3	Problem size minimization and solution optimization	226
5.6.4	Numerical considerations	227
5.6.5	Design flow	228
	References	230
6	Practical HF/VHF/UHF RF power amplifier realization	232
	Daniel P. Myer	
6.1	Introduction	232
6.2	RF power amplifier markets	232
6.3	The realization process	233
6.3.1	RFPA qualitative specification delineation	234
6.3.2	RFPA specifications, generic list and quantification guidelines	236
6.3.3	Specification/hardware realization	241
6.4	RFPA system level design overview	242
6.4.1	RF power amplifier module design overview	243
6.4.2	RF power transistor device selection process guidelines	246
6.4.3	RF power transistor bias/thermal tracking networks	249
6.4.4	RF input/output coupling/decoupling networks	250
6.4.5	Power transistor impedance matching	250
6.4.6	Feedback networks	251
6.4.7	Thermal management	251
6.5	Hypothetical amplifier design example	252
6.5.1	Hypothetical application example overview	252
6.5.2	Amplifier qualitative specification delineation	252
6.5.3	Amplifier specification quantification	253
6.5.4	Amplifier hardware design/realization	254
6.5.5	RF transistor selection	255
6.5.6	Gate bias/temperature tracking/compensation network	257
6.5.7	Input/output RF/DC coupling/decoupling networks	259
6.5.8	Input/output impedance matching networks	259
6.5.9	Feedback network	267
6.5.10	Test setup configuration/analysis	268
6.5.11	Physical RFPA module construction	271
6.5.12	RFPA module test results	273
6.5.13	Beyond the test data	281
	References	283

7	Microwave hybrid amplifier realization	284
	Dominic FitzPatrick	
7.1	Introduction	284
7.2	Printed circuit boards	285
7.3	Housing	293
7.3.1	Materials	294
7.3.2	Sealing and hermeticity	294
7.3.3	Construction	299
7.3.4	Thermal issues and heat sinking	305
7.3.5	RF connections	311
7.4	Components	315
7.4.1	Passive – lumped components	315
7.4.2	Passive – distributed components	323
7.4.3	Transistors	331
7.5	Amplifier design	333
7.5.1	Topologies	333
7.5.2	Matching and stability	336
7.5.3	Internally matched device amplifiers	343
7.5.4	Combining	344
7.5.5	Module size/system integration	344
7.6	Biasing and control	345
7.6.1	Control and interfacing	352
7.7	Tuning techniques	353
	References	355
8	Monolithic power amplifiers	357
	Inder J. Bahl	
8.1	Overview of MMIC power amplifiers	357
8.1.1	Brief history of MMIC power amplifiers	357
8.1.2	Advantages of monolithic power amplifiers	358
8.2	Monolithic IC technology	359
8.2.1	MMIC fabrication	360
8.2.2	MMIC substrates	361
8.2.3	MMIC active devices	361
8.2.4	MMIC matching elements	362
8.3	MMIC design methodology	370
8.3.1	CAD tools	370
8.3.2	Design procedure	371
8.3.3	EM simulators	372
8.4	MMIC PA summary and examples	372
8.4.1	Narrowband power amplifier	374
8.4.2	Broadband power amplifiers	376
8.4.3	Ultra broadband power amplifiers	377
8.4.4	High-power amplifiers	381

Contents

8.4.5	Millimeter-wave 2.4W PA	386
8.4.6	Wireless 3W power amplifier	386
8.4.7	High-voltage monolithic PAs	387
8.5	Packaging of MMIC PAs	389
8.5.1	Ceramic packages	390
8.5.2	Plastic packages	394
8.5.3	Package assembly	396
8.6	MMIC power amplifier characterization	401
	References	406
9	RF power amplifier thermal design	411
	Mali Mahalingam	
9.1	Why thermal design deserves careful attention?	411
9.2	RFPA thermal design – basics	413
9.2.1	RFPA thermal design in a typical portable product	413
9.2.2	RFPA thermal design in a typical radio base station	416
9.2.3	Basic heat transfer processes and their role in an RFPA thermal performance	419
9.3	Thermo-physical properties of materials in an RFPA	423
9.4	Tools to characterize and predict the thermal performance of RFPAs	427
9.5	RFPA thermal design and management – advanced	432
9.6	RFPA thermal design – trends and prognostication	440
	References	442
10	Reliability	446
	Bill Roesch	
10.1	Introduction	446
10.2	Vocabulary and definitions (units, goals, and strategy)	447
10.2.1	Reliability goals	448
10.2.2	Semiconductor reliability strategy	448
10.3	Failure criteria	449
10.4	Failure modes	450
10.5	Failure mechanisms	451
10.5.1	Metalization	451
10.5.2	Dielectric	453
10.5.3	Bulk substrate material	454
10.5.4	Schottky gate FET failure causes	454
10.6	Failure distributions	455
10.7	Acceleration factors	458
10.7.1	Thermal acceleration	458
10.7.2	Current acceleration	462
10.7.3	Voltage acceleration factors	465
10.7.4	RF bias acceleration	472

10.8	Reliability predictions (MTBF, MTTF, FITs, etc.)	473
10.9	Wear-out versus defects (acceleration versus real life)	475
10.9.1	Thermal excursion example no. 1. Interconnect vias	475
10.9.2	Thermal excursion example no. 2. Copper bump	478
10.9.3	Defect amplification and K factors	482
10.9.4	Environmental example – humidity activation energy	488
10.10	Process effects and influence	492
10.11	Design for reliability	495
10.12	Historical trends and technology comparisons	501
10.13	Summary	502
	References	505
11	Power amplifier applications	508
	Mustafa Akkul and Wolfgang Bösch	
11.1	Introduction	508
11.2	System design parameter tradeoffs	509
11.2.1	Output power–efficiency tradeoff	509
11.2.2	Linearity, modulation scheme, and crest factor	512
11.3	System level linearization techniques	514
11.3.1	Introduction to linearization techniques	514
11.3.2	Digital baseband predistortion	514
11.3.3	Memory effect compensation	517
11.3.4	Impact on power efficiency	517
11.4	Wireless communication power amplifiers	519
11.4.1	Mobile radio communication today	519
11.4.2	System level and power amplifier requirements	522
11.4.3	Power amplifier design outline	523
11.4.4	Doherty amplifier for efficient base stations	527
11.5	Military power amplifiers	530
11.5.1	Radar Tx/Rx modules	530
11.5.2	EW applications	534
11.5.3	Anti-IED applications	538
11.6	In-phase power combining techniques	538
11.6.1	Wilkinson power combiners	538
11.6.2	Gysel combiner	542
11.7	Quadrature-phase power combining – balanced amplifiers	544
11.7.1	Branch-line quadrature hybrid [19]	547
11.7.2	Lange coupler	549
11.8	Anti-phase power combining – push–pull amplifiers	552
11.8.1	Coupled coil transformers	553
11.8.2	Transmission line transformers	554
11.8.3	RF/microwave push–pull amplifier	557

Contents

11.9	Doherty combining	559
11.10	Conclusions	567
	References	568
12	Amplifier measurements	570
	Michael G. Hiebel	
12.1	Introduction	570
12.2	Power measurements	570
12.2.1	Typical power sensor principles	570
12.2.2	Typical sources of measurement uncertainties	574
12.2.3	High-power RF measurements and directional power	576
12.2.4	Power measurements using a spectrum analyzer	579
12.3	S-parameter measurements	580
12.3.1	The concept of S-parameters	580
12.3.2	Scalar network analyzers and their limitations	582
12.3.3	Vector network analyzers	586
12.3.4	Introduction to system error correction	588
12.3.5	Calibration with different connector types	589
12.3.6	Calibration with PCBs, test fixtures, and wafer probers	593
12.3.7	Calibration consideration for high-power setups	596
12.3.8	Residual errors and measurement uncertainties	598
12.4	Further linear measurements	599
12.4.1	Amplifier gain definitions	599
12.4.2	Efficiency factor	602
12.4.3	Linear distortion, phase and group delay measurement	603
12.4.4	Linear stability considerations	605
12.4.5	Mixed-mode S-parameters	608
12.5	Nonlinear measurements	611
12.5.1	Inter modulation distortion (IMD) and harmonic distortion (HMD)	611
12.5.2	Compression point	615
12.5.3	Large-signal network analysis	616
12.5.4	Load- and source-pull measurements	619
12.5.5	Hot S-parameters	622
12.6	Modulated measurements	623
12.6.1	Crest factor and CCDF	624
12.6.2	Adjacent channel power ratio (ACPR)	625
12.6.3	Noise-power ratio (NPR)	630
12.6.4	Error vector magnitude (EVM) and constellation diagram	630
12.6.5	AM/AM and AM/PM measurements	632
12.6.6	Memory effects	632

Contents

12.6.7 Pulsed measurements	633
12.6.8 Bit error ratio (BER) and symbol error ratio (SER)	635
12.7 Noise measurements	636
12.7.1 Amplifier noise factor and noise figure	637
12.7.2 Noise figure measurement	637
12.7.3 Noise parameters	640
12.8 Conclusions	641
References	642
<i>About the authors</i>	644
<i>Index</i>	651