

Contents

About the Authors	xiii
Acknowledgements	xv
Foreword	xvii
Preface	xix
Nomenclature	xxiii
Chapter 1 Introduction	1
1.1 Historical Context	1
1.2 The Laws of Electromagnetism	4
1.2.1 <i>Ampere's Magnetic Circuit Law</i>	4
1.2.2 <i>Faraday's Law of Electromagnetic Induction</i>	5
1.3 Ferromagnetic Materials	7
1.4 Losses in Magnetic Components	10
1.4.1 <i>Copper Loss</i>	10
1.4.2 <i>Hysteresis Loss</i>	11
1.4.3 <i>Eddy Current Loss</i>	13
1.4.4 <i>Steinmetz Equation for Core Loss</i>	14
1.5 Magnetic Permeability	14
1.6 Magnetic Materials for Power Electronics	16
1.6.1 <i>Soft Magnetic Materials</i>	17
1.6.2 <i>The Properties of some Magnetic Materials</i>	19
1.7 Problems	21
References	21
Further Reading	21
SECTION I INDUCTORS	23
Chapter 2 Inductance	25
2.1 Magnetic Circuits	25
2.2 Self and Mutual Inductance	30
2.3 Energy Stored in the Magnetic Field of an Inductor	34

2.3.1	<i>Why Use a Core?</i>	35
2.3.2	<i>Distributed Gap</i>	38
2.4	Self and Mutual Inductance of Circular Coils	39
2.4.1	<i>Circular Filaments</i>	39
2.4.2	<i>Circular Coils</i>	40
2.5	Fringing Effects around the Air Gap	48
2.6	Problems	51
	References	53
	Further Reading	54
Chapter 3	Inductor Design	55
3.1	The Design Equations	55
3.1.1	<i>Inductance</i>	55
3.1.2	<i>Maximum Flux Density</i>	55
3.1.3	<i>Winding Loss</i>	56
3.1.4	<i>Optimum Effective Permeability</i>	57
3.1.5	<i>Core Loss</i>	58
3.1.6	<i>The Thermal Equation</i>	58
3.1.7	<i>Current Density in the Windings</i>	59
3.1.8	<i>Dimensional Analysis</i>	61
3.2	The Design Methodology	61
3.3	Design Examples	64
3.3.1	<i>Example 3.1: Buck Converter with a Gapped Core</i>	64
3.3.2	<i>Example 3.2: Forward Converter with a Toroidal Core</i>	69
3.4	Multiple Windings	74
3.4.1	<i>Example 3.3: Flyback Converter</i>	75
3.5	Problems	84
	References	89
	Further Reading	89
SECTION II	TRANSFORMERS	93
Chapter 4	Transformers	95
4.1	Ideal Transformer	96
4.1.1	<i>No Load Conditions</i>	97
4.1.2	<i>Load Conditions</i>	98
4.1.3	<i>Dot Convention</i>	99
4.1.4	<i>Reflected Impedance</i>	100
4.1.5	<i>Summary</i>	101
4.2	Practical Transformer	102
4.2.1	<i>Magnetizing Current and Core Loss</i>	102
4.2.2	<i>Winding Resistance</i>	105
4.2.3	<i>Magnetic Leakage</i>	105
4.2.4	<i>Equivalent Circuit</i>	107
4.3	General Transformer Equations	109

4.3.1	<i>The Voltage Equation</i>	109
4.3.2	<i>The Power Equation</i>	112
4.3.3	<i>Winding Loss</i>	113
4.3.4	<i>Core Loss</i>	114
4.3.5	<i>Optimization</i>	114
4.4	Power Factor	116
4.5	Problems	121
	References	122
	Further Reading	122
Chapter 5	Transformer Design	123
5.1	The Design Equations	124
5.1.1	<i>Current Density in the Windings</i>	124
5.1.2	<i>Optimum Flux Density unlimited by Saturation</i>	125
5.1.3	<i>Optimum Flux Density limited by Saturation</i>	126
5.2	The Design Methodology	128
5.3	Design Examples	129
5.3.1	<i>Example 5.1: Centre-Tapped Rectifier Transformer</i>	129
5.3.2	<i>Example 5.2: Forward Converter</i>	134
5.3.3	<i>Example 5.3: Push-Pull Converter</i>	140
5.4	Transformer Insulation	146
5.4.1	<i>Insulation Principles</i>	147
5.4.2	<i>Practical Implementation</i>	147
5.5	Problems	148
	Further Reading	155
Chapter 6	High Frequency Effects in the Windings	159
6.1	Skin Effect Factor	160
6.2	Proximity Effect Factor	163
6.2.1	<i>AC Resistance in a Cylindrical Conductor</i>	165
6.3	Proximity Effect Factor for an Arbitrary Waveform	171
6.3.1	<i>The Optimum Thickness</i>	174
6.4	Reducing Proximity Effects by Interleaving the Windings	182
6.5	Leakage Inductance in Transformer Windings	184
6.6	Problems	187
	References	193
	Further Reading	193
Chapter 7	High Frequency Effects in the Core	197
7.1	Eddy Current Loss in Toroidal Cores	197
7.1.1	<i>Numerical Approximations</i>	200
7.1.2	<i>Equivalent Core Inductance</i>	201
7.1.3	<i>Equivalent Core Resistance</i>	202
7.2	Core Loss	204
7.3	Complex Permeability	209
7.4	Laminations	212

7.5	Problems	214
	References	216
	Further Reading	216
SECTION III ADVANCED TOPICS		219
Chapter 8 Measurements		221
8.1	Measurement of Inductance	221
	8.1.1 <i>Step Voltage Method</i>	222
	8.1.2 <i>Incremental Impedance Method</i>	223
8.2	Measurement of the <i>B-H</i> Loop	225
8.3	Measurement of Losses in a Transformer	227
	8.3.1 <i>Short-Circuit Test (Winding/Copper Loss)</i>	228
	8.3.2 <i>Open-Circuit Test (Core/Iron Loss)</i>	229
	8.3.3 <i>Core Loss at High Frequencies</i>	232
	8.3.4 <i>Leakage Impedance at High Frequencies</i>	235
8.4	Capacitance in Transformer Windings	237
	8.4.1 <i>Transformer Effective Capacitance</i>	238
	8.4.2 <i>Admittance in the Transformer Model</i>	239
8.5	Problems	244
	References	245
	Further Reading	245
Chapter 9 Planar Magnetics		247
9.1	Inductance Modelling	248
	9.1.1 <i>Spiral Coil in Air</i>	249
	9.1.2 <i>Spiral Coil on a Ferromagnetic Substrate</i>	253
	9.1.3 <i>Spiral Coil in a Sandwich Structure</i>	261
9.2	Fabrication of Spiral Inductors	265
	9.2.1 <i>PCB Magnetics</i>	265
	9.2.2 <i>Thick Film Devices</i>	267
	9.2.3 <i>LTCC Magnetics</i>	270
	9.2.4 <i>Thin Film Devices</i>	271
	9.2.5 <i>Summary</i>	274
9.3	Problems	275
	References	298
	Further Reading	299
Chapter 10 Variable Inductance		301
10.1	Saturated Core Inductor	303
10.2	Swinging Inductor	309
10.3	Sloped Air Gap Inductor	312
10.4	Applications	315
	10.4.1 <i>Power Factor Correction</i>	315
	10.4.2 <i>Harmonic Control with Variable Inductance</i>	317

10.4.3	<i>Maximum Power Point Tracking</i>	323
10.4.4	<i>Voltage Regulation</i>	329
10.5	Problems	331
	References	335
	Further Reading	335
	Appendix A	337
	Index	341