

CONTENTS

Preface xi

CHAPTER I Basic Electromagnetic Concepts

I.0	Introduction	3
I.1	Electric Circuit Concepts	3
I.1.1	Electric Potential	3
I.1.2	Complex Numbers	7
I.1.3	Electric Field Parameters	10
I.1.4	Basic Elements	11
I.1.5	Impedance	32
I.1.6	Principles of Electric Circuits	35
I.1.7	Power of a Single-Phase Source	41
I.1.8	Power Factor	47
I.1.9	Effects of the Power Factor	49
I.1.10	Power-Factor Improvement	51
I.1.11	Harmonics	57
I.1.12	Theorems	61
I.2	Magnetic Circuit Concepts	64
I.2.1	Magnetic Flux	64
I.2.2	Magnetic Flux Density	69
I.2.3	Magnetomotive Force	70
I.2.4	Magnetic Field Intensity	71
I.2.5	The B - H Curve and Magnetic Domains	75
I.2.6	Permeability	78
I.2.7	Reluctance	82
I.2.8	The Concept of Generated Voltage	85
I.2.9	Energy Content of Magnetic Materials	93
I.2.10	Principles of Magnetic Circuits	95
I.2.11	Magnetic Losses	103
I.2.12	Equivalent Circuit of a Coil	109
I.2.13	Mathematical Relationships of Self- and Mutual Inductances	111
I.2.14	Polarity and Equivalent Circuits of Magnetically Coupled Coils	119
I.2.15	Force, Energy, and Torque	123
I.3	Force, Energy, and Torque	125
I.3.1	Force Exerted by an Electromagnet	127
I.3.2	Energy Stored in the Magnetic Field of Coils	131

1.3.3	Torque Developed by Rotating Transducers	133
1.3.4	Applications of Electromagnetism	134
1.4	Summary	135
1.5	Review Questions	143
1.6	Problems	143

CHAPTER 2 Transformers **151**

2.0	Introduction	153
2.1	Single-Phase Transformers	154
2.1.1	Principle of Operation	155
2.1.2	Ideal Transformer Relationships	157
2.1.3	Derivation of the Equivalent Circuit	160
2.1.4	Waveform of Excitation Current	169
2.1.5	Components of Primary Current and Corresponding Fluxes	171
2.1.6	Transformer Characteristics	173
2.1.7	Per-Unit Values	178
2.2	Three-Phase, Two-Winding Transformers	188
2.2.1	Introduction	188
2.2.2	Review of Three-Phase Systems	189
2.2.3	One-Line Diagram	193
2.2.4	Types of Three-Phase Transformers	194
2.2.5	Harmonics of the Exciting Current	210
2.3	Autotransformers	211
2.4	Parallel Operation of Transformers	219
2.4.1	Transformers Must Have Equal Leakage Impedances	220
2.4.2	Transformers Must Have Equal Turns Ratios	220
2.4.3	Equal Phase Shift Between the Voltages of Paralleled Units	221
2.4.4	Same Phase Rotation	222
2.5	Instrument Transformers and Wiring Diagrams	225
2.5.1	Instrument Transformers	225
2.5.2	Wiring Diagrams	230
2.6	Transformer's Nameplate Data	236
2.7	Conclusion	238
2.8	Summary	239
2.9	Review Questions	243
2.10	Problems	244

CHAPTER 3 Three-Phase Induction Machines **249**

3.0	Introduction	251
3.1	Three-Phase Induction Motors	251
3.1.1	Stator and Rotor	251
3.1.2	Principles of Operation	255

3.1.3	Rotating Magnetic Field	256
3.1.4	Slip	261
3.1.5	Equivalent Circuit	264
3.1.6	Torque and Power Relationships	269
3.2	Industrial Considerations	277
3.2.1	Classification of Induction Motors	277
3.2.2	Mechanical Loads	279
3.2.3	Mechanical Load Changes and Their Effects on a Motor's Parameters	281
3.2.4	Voltage, Efficiency, and Power-Factor Considerations	282
3.3	Measurement of Equivalent-Circuit Parameters	290
3.4	Asynchronous Generators	298
3.5	Controls	302
3.5.1	Reduction of the Motor's High Starting Current and Torque	302
3.5.2	Variable Frequency Drives	307
3.5.3	Soft Start	317
3.5.4	Plugging	319
3.6	Conclusion	319
3.7	Tables	320
3.8	Review Questions	324
3.9	Problems	325

CHAPTER 4 Single-Phase Motors

331

4.0	Introduction	332
4.1	Revolving Fields	333
4.1.1	Rotor Stationary	334
4.1.2	Rotor Turning	334
4.2	Equivalent Circuit	334
4.3	Torque Developed	335
4.4	Methods of Starting	337
4.4.1	Auxiliary Winding, Permanently Connected	337
4.4.2	Auxiliary Winding with Capacitor Start	339
4.4.3	Auxiliary Winding, Removed After Starting	340
4.4.4	Auxiliary Winding, with a Starting and a Running Capacitor	341
4.5	Magnetic Fields at Starting	341
4.6	Types of 1-ϕ Motors	345
4.6.1	Split-phase	345
4.6.2	Shaded-Pole Motors	346
4.6.3	Revolving Field	346
4.6.4	Stepper Motors	347
4.6.5	Control	348
4.6.6	Series AC/DC Motors	349

- 4.7 Conclusion 350
- 4.8 Problems 351

CHAPTER 5 Synchronous Machines

353

- 5.0 Three-Phase Synchronous Machines 354
- 5.1 Three-Phase Cylindrical Rotor Machines: Motors 355
 - 5.1.1 Rotor 359
 - 5.1.2 Rotating Fields 359
 - 5.1.3 Principle of Operation 361
 - 5.1.4 Starting 362
 - 5.1.5 Equivalent Circuits 363
 - 5.1.6 Field Current 366
 - 5.1.7 Phasor Diagrams 367
 - 5.1.8 Power and Torque Developed 374
 - 5.1.9 Effects of Field Current on the Characteristics of the Motor 378
- 5.2 Three-Phase Cylindrical Rotor Machines: Generators 389
 - 5.2.1 Equivalent-Circuit and Phasor Diagrams 389
 - 5.2.2 Regulator of Alternators 392
 - 5.2.3 Characteristics of Alternators 393
 - 5.2.4 Measurement of Parameters 397
- 5.3 Salient-Pole Synchronous Machines 405
 - 5.3.1 Introduction 405
 - 5.3.2 Phasor Diagrams 407
 - 5.3.3 Power Developed 409
 - 5.3.4 Torque Angle for Maximum Power 411
 - 5.3.5 Stiffness of Synchronous Machines 412
- 5.4 Conclusion 416
- 5.5 Review of Important Mathematical Relationships 418
- 5.6 Manufacturer's Data 420
- 5.7 Review Questions 422
- 5.8 Problems 422

CHAPTER 6 DC Machines

425

- 6.0 Introduction 426
- 6.1 Steady-State Analysis 427
 - 6.1.1 General 427
 - 6.1.2 Principles of Operation 429
 - 6.1.3 Power Considerations 433
 - 6.1.4 Voltage and Torque Relationships as Functions of Mutual Inductance 436
 - 6.1.5 Magnetic System, Flux Distribution, and Armature Reaction 438
 - 6.1.6 Commutation 442
 - 6.1.7 Equivalent Circuits and External Machine Characteristics 444

6.1.8	Starting	462	
6.1.9	Open-Circuit Characteristics and DC Generators	464	
6.2	Modern Methods of Speed Control	477	
6.2.1	Rectifiers	477	
6.2.2	Single-Phase, Full-Wave Controlled Rectifiers	478	
6.2.3	Three-Phase, Full-Wave Controlled Rectifiers	481	
6.3	Conclusion	489	
6.4	Review Questions	493	
6.5	Problems	493	

CHAPTER 7 Control Schematics **497**

7.0	Introduction	498	
7.1	Basic Devices and Symbols	499	
7.1.1	Electromagnetic Relays	499	
7.1.2	Thermal Overload Relays	503	
7.1.3	Electrical Contacts	504	
7.1.4	Indicating Lights	506	
7.1.5	Start-Stop Pushbuttons	506	
7.1.6	Industrial Timers	507	
7.1.7	Temperature Sensors	509	
7.2	The Concept of Protection	512	
7.2.1	General	512	
7.2.2	Protective Devices	514	
7.3	Actual Control Schematics	519	
7.3.1	Control Schematics of Three-Phase Induction Motors	519	
7.3.2	Synchronous Motors	524	
7.4	Conclusion	530	
7.5	Review Questions	533	
7.6	Problems	533	

CHAPTER 8 Electrical Safety and Reduction in Energy Consumption **537**

8.1	Electrical Safety	539	
8.1.1	Introduction	539	
8.1.2	Basic Protective Devices	540	
8.1.3	Grounding Systems	542	
8.1.4	The Utility's Ground	542	
8.1.5	Residence's Ground	543	
8.1.6	Equipment's Enclosure Ground	543	
8.1.7	Bonding	543	
8.1.8	Ground Resistance	544	
8.1.9	Short Circuits	544	