
Contents

Preface.....	xix
Author.....	xxv
1. Measurement Systems.....	1
1.1 Introduction.....	1
1.2 Measurement System Architecture.....	1
1.2.1 Sensor Dynamics.....	3
1.2.2 Overview of Signal Conditioning.....	7
1.3 Errors in Measurements.....	7
1.4 Standards Used in Measurements.....	14
1.4.1 Introduction.....	14
1.4.2 Electrical Standards.....	14
1.4.2.1 Volt.....	15
1.4.2.2 Resistance.....	19
1.4.2.3 Current and Charge.....	25
1.4.2.4 Capacitance.....	28
1.4.2.5 Inductance.....	31
1.4.3 Time and Frequency Standards.....	32
1.4.4 Physical Standards.....	33
1.4.4.1 Mass.....	33
1.4.4.2 Length.....	35
1.4.4.3 Temperature.....	35
1.4.4.4 Uncertainties in the SI Base Units.....	35
1.5 Chapter Summary.....	36
Problems.....	36
2. Analog Signal Conditioning in Instrumentation.....	41
2.1 Introduction.....	41
2.2 Differential Amplifiers.....	41
2.2.1 Introduction.....	41
2.2.2 Analysis of Differential Amplifiers.....	42
2.2.3 Common-Mode Rejection Ratio.....	43
2.2.4 Measurement of CMRR, A_D , and A_C	44
2.2.5 Effect of Source Resistance Asymmetry on CMRR.....	44
2.3 Operational Amplifiers.....	47
2.3.1 Types of Op-Amps.....	48
2.3.2 Basic Broadband Amplifier Design Using Op-Amps.....	50
2.3.2.1 Noninverting Amplifier.....	50
2.3.2.2 Inverting Amplifier and Summer.....	52
2.3.3 Current Feedback Op-Amps.....	53
2.4 Analog Active Filter Applications Using Conventional Op-Amps.....	58
2.4.1 Introduction.....	58

2.4.2	Analog Active Filter Architectures	59
2.4.2.1	Controlled-Source Active Filters	59
2.4.2.2	Biquad Active Filters	62
2.4.2.3	Generalized Impedance Converter Active Filters	65
2.4.2.4	High-Order Active Filters	69
2.4.3	Operational Amplifier Integrators and Differentiators.....	69
2.4.4	Summary.....	71
2.5	Instrumentation Amplifiers.....	71
2.5.1	Instrumentation Amplifiers That Can Be Made from Op-Amps	73
2.5.2	Isolation Amplifiers	75
2.5.3	Autozero Amplifiers	77
2.5.4	Absolute Isolation	79
2.5.5	Summary.....	79
2.6	Nonlinear Analog Signal Processing by Op-Amps and by Special Function Modules	81
2.6.1	Introduction.....	81
2.6.2	Precision Absolute Value Circuits	83
2.6.3	Multifunction Converters	85
2.6.4	True RMS-to-DC Converters.....	86
2.6.5	Square-Root Circuits and Dividers	88
2.6.6	Peak Detectors and Track-and-Hold Circuits	90
2.6.7	Log Ratio and Trigonometric ICs	94
2.6.8	Summary.....	95
2.7	Charge Amplifiers.....	96
2.7.1	Introduction.....	96
2.7.2	Charge Amplifiers Used with Piezoelectric Transducers.....	96
2.7.3	Charge Amplifier as an Integrating Coulombmeter	98
2.8	Phase-Sensitive Rectifiers	100
2.8.1	Introduction	100
2.8.2	Double-Sideband, Suppressed-Carrier Modulation	100
2.8.3	Demodulation of DSBSCM Signals by Analog Multiplier.....	101
2.8.4	Other PSR Designs.....	102
2.8.5	Lock-In Amplifier.....	102
2.8.5.1	Introduction	102
2.8.5.2	Calculation of the SNR Improvement Using a Lock-In Amplifier	107
2.8.5.3	Summary	110
2.8.6	Signal Averaging to Improve SNR of Evoked Transient Signals	111
2.8.6.1	Introduction	111
2.8.6.2	Analysis of SNR Improvement by Averaging.....	113
2.9	Chapter Summary.....	116
	Problems.....	116
3.	Noise and Coherent Interference in Measurements	125
3.1	Introduction	125
3.2	Descriptions of Random Noise in Circuits	125
3.2.1	Probability Density Functions	126

3.2.2	Power Density Spectrum	127
3.2.3	Sources of Noise in Signal Conditioning Systems	130
3.2.3.1	Noise from Resistors	130
3.2.3.2	Two-Source Noise Model for Active Devices	133
3.2.3.3	Noise in JFETs	134
3.2.3.4	Noise in BJTs	135
3.3	Propagation of Gaussian Noise through Linear Filters	137
3.4	Broadband Noise Factor and Noise Figure of Amplifiers	138
3.5	Spot Noise Factor and Figure	140
3.6	Transformer Optimization of Amplifier F_{spot} and Output SNR	143
3.7	Cascaded Noisy Amplifiers	144
3.8	Examples of Calculations of the Noise-Limited Resolution of Certain Signal Conditioning Systems	145
3.8.1	Calculation of the Minimum Resolvable AC Input Voltage to a Noisy, Inverting Op-Amp Amplifier	145
3.8.2	Calculation of the Minimum Resolvable Direct Current in White and $1/f$ Noise	147
3.8.3	Calculation of the Minimum Resolvable AC Input Signal to Obtain a Specified Output SNR in a Transformer-Coupled, Tuned Amplifier	148
3.8.4	Calculation of the Smallest $\Delta R/R$ in a Wheatstone Bridge to Give a Specified SNR_{out}	149
3.8.5	Determination of the Conditions for Maximum Output SNR Given a Simple Inverting Op-Amp Amplifier with Known e_{na} and i_{na}	151
3.9	Modern, Low-Noise Amplifiers for Use in Instrumentation Signal-Conditioning Systems	151
3.10	Coherent Interference and Its Minimization	153
3.10.1	Sources of Coherent Interference	153
3.10.1.1	Direct Electrostatic Coupling of Coherent Interference	154
3.10.1.2	Direct Magnetic Induction of Coherent Interference	155
3.10.1.3	Ground Loops	157
3.10.2	Cures for Coherent Interference	158
3.10.2.1	Powerline Low-Pass Filters	158
3.10.2.2	Transient Voltage Suppressors	159
3.10.2.3	Coherent Interference Induced in Coaxial Cables by Magnetic Coupling	164
3.10.2.4	Single Grounding of Coax Shields to Prevent Ground-Loop Interference	165
3.10.2.5	Use of a Longitudinal Choke or Neutralizing Transformer to Attenuate Common-Mode Coherent Interference	166
3.10.2.6	Experimental Verification of Cabling and Grounding Schemes to Achieve Minimum Noise Pickup	168
3.10.2.7	Circuit Grounding	170
3.10.2.8	Ferrite Beads and Feedthrough Capacitors	170
3.10.2.9	Interruption of Ground Loops by the Use of Isolation Transformers and Photooptic Couplers	171

3.10.2.10 Photooptic Couplers	172
3.10.2.11 Use of Guarding and Shielding to Reduce Common-Mode Coherent Interference	173
3.10.3 Summary of Techniques for Coherent Noise Reduction	177
3.11 Chapter Summary.....	179
Problems.....	180
4. DC Null Methods of Measurement	187
4.1 Introduction	187
4.2 Wheatstone Bridge Analysis	189
4.3 Kelvin Bridge	190
4.4 Anderson Constant Current Loop.....	193
4.4.1 Introduction.....	193
4.4.2 Anderson Loop Applied to Groups of Sensors	195
4.4.3 Conclusion	201
4.5 Potentiometers.....	201
4.6 Chapter Summary.....	202
Problems.....	203
5. AC Null Measurements	209
5.1 Introduction	209
5.2 Components: Inductor Equivalent Circuits.....	209
5.3 Components: Capacitor Equivalent Circuits.....	211
5.4 AC Operation of Wheatstone Bridges	213
5.5 AC Bridges	214
5.5.1 Bridges Used to Measure Capacitance.....	215
5.5.1.1 Resistance Ratio Bridge.....	215
5.5.1.2 Schering Bridge	216
5.5.1.3 Parallel C Bridge	217
5.5.1.4 De Sauty Bridge	218
5.5.1.5 Wien Bridge	219
5.5.1.6 Commutated Capacitor Bridge	221
5.5.2 Bridges Used to Measure Inductance and Mutual Inductance.....	222
5.5.2.1 Maxwell Bridge.....	223
5.5.2.2 Parallel Inductance Bridge	224
5.5.2.3 Hay Bridge.....	224
5.5.2.4 Owen Bridge.....	225
5.5.2.5 Anderson Bridge.....	226
5.5.2.6 Heaviside Mutual Inductance Bridge.....	227
5.5.2.7 Heydweiller Mutual Inductance "Bridge"	228
5.5.3 Null Method of Measuring Transistor Small-Signal Transconductance and Feedback Capacitance	229
5.6 Chapter Summary.....	232
Problems.....	232
6. Survey of Sensor Mechanisms	237
6.1 Introduction	237
6.2 Categories of Sensor Mechanisms.....	237
6.2.1 Resistive Sensors	237

Contents

6.2.1.1	Resistive Temperature Sensors.....	238
6.2.1.2	Resistive Strain Gauges	241
6.2.1.3	Photoconductors.....	242
6.2.1.4	Conductive Relative Humidity Sensors.....	246
6.2.1.5	Direct Resistance Change Used to Sense Position or Angle	248
6.2.1.6	Sensors Based on the Giant Magnetoresistive Effect.....	250
6.2.1.7	Anisotropic Magnetoresistance	253
6.2.2	Voltage-Generating Sensors	260
6.2.2.1	Thermocouples and Thermopiles	260
6.2.2.2	Photovoltaic Cells	263
6.2.2.3	Piezoelectric Transducers.....	266
6.2.2.4	Pyroelectric Sensors.....	270
6.2.3	Sensors Whose Voltage Output Is Proportional to $d\Phi/dt$	274
6.2.3.1	Variable Reluctance Phonograph Pickup.....	275
6.2.3.2	Electrodynamic Accelerometer	276
6.2.3.3	Linear Velocity Sensors	277
6.2.4	Sensors Whose Output EMF Depends on the Interaction of a Magnetic Field with Moving Charges.....	278
6.2.4.1	Faraday Effect Flowmeters	278
6.2.4.2	Hall Effect Sensors	281
6.2.5	Sensors Based on Variable Magnetic Coupling.....	284
6.2.5.1	LVDT	284
6.2.5.2	Synchros and Resolvers.....	286
6.2.6	Variable Capacitance Sensors.....	288
6.3	Fiber-Optic Sensors.....	291
6.3.1	Magneto-Optic Current Sensors.....	292
6.3.2	Means of Measuring the Optical Rotation of the Linearly Polarized Light Output of Certain Optical Sensors	295
6.3.3	Fiber-Optic Mechanosensors	306
6.4	Photomultiplier Tubes and Related Photoelectron Multiplication Devices	311
6.4.1	Introduction.....	311
6.4.2	Operation of PMTs.....	313
6.4.3	Single-Channel Photomultiplier.....	316
6.4.4	Microchannel-Plate Photomultipliers	317
6.4.5	Summary.....	319
6.5	Ionizing Radiation Sensors.....	319
6.5.1	Introduction.....	319
6.5.2	Geiger-Muller Tubes	320
6.5.3	Solid-State, Crystal Radiation Sensors.....	322
6.5.4	Scintillation Counters.....	326
6.6	Electrochemical Sensors	327
6.6.1	Introduction.....	327
6.6.2	pH- and Ion-Specific Electrodes	328
6.6.3	Polarographic Electrodes	330
6.6.4	Fuel Cell Electrodes.....	332
6.7	Mechano-Optical Sensors.....	332
6.7.1	Introduction.....	332
6.7.2	Optical Coding Disks.....	333

6.7.3	Sagnac Effect Sensing of Angular Velocity.....	334
6.7.4	Laser Doppler Velocimetry	338
6.8	Chapter Summary.....	345
	Problems.....	345
7.	Applications of Sensors to Physical Measurements	361
7.1	Introduction.....	361
7.2	Measurement of Angular Acceleration, Velocity, and Displacement.....	361
7.2.1	Angular Acceleration Measurement.....	361
7.2.1.1	Angular Acceleration Measurement with a Constrained Mechanical Gyro	362
7.2.1.2	Simple Inertia Wheel–Spring–Dashpot Angular Accelerometer	363
7.2.1.3	Servoangular Accelerometer	364
7.2.2	Angular Velocity Measurement with Mechanical Gyroscopes.....	365
7.2.2.1	Mechanical Rate Gyro	369
7.2.2.2	Sagnac-Effect Fiber-Optic Gyroscopes.....	372
7.2.2.3	Vibrating Mass Rate Gyro.....	374
7.2.2.4	Humphrey Air Jet Rate Gyro.....	377
7.2.3	Angular Velocity Measurement with Tachometers.....	381
7.2.4	Angular Position Measurement with Gyroscopes.....	386
7.2.5	Angular Position Measurement with Clinometers.....	391
7.2.6	Angular Position Measurement of Shafts	394
7.3	Measurement of Linear Acceleration, Velocity, Displacement, and Position	396
7.3.1	Accelerometers	396
7.3.1.1	Basic Newtonian Accelerometer	396
7.3.1.2	Servoaccelerometer Design.....	397
7.3.1.3	Piezoelectric Accelerometers	398
7.3.2	Linear Velocity Measurement.....	400
7.3.2.1	Means of Measurement of Fluid Velocity	401
7.3.2.2	Other Means of Measuring Fluid Velocity and Flow	404
7.3.3	Measurement of Linear Position.....	415
7.3.3.1	Introduction	415
7.3.3.2	GPS Background.....	420
7.3.3.3	Use of the Global Positioning System to Locate Objects in Three Dimensions	421
7.3.3.4	GPS System Development.....	423
7.3.3.5	GPS Signals	425
7.3.3.6	GPS Hardware	426
7.3.3.7	GPS Tag Applications in Biology	430
7.3.3.8	GPS Summary.....	430
7.3.4	Use of Optical Interferometry to Measure Δx	431
7.3.4.1	Introduction	431
7.3.4.2	Measurement of Tympanal Membrane Displacement by Fiber-Optic Fizeau Interferometer.....	438
7.3.4.3	Measurement of Skin Vibration by Optical Interferometry...	439
7.3.4.4	Two-Frequency, Heterodyne Interferometry	442
7.3.4.5	Fabry–Pérot Interferometer.....	444
7.3.4.6	Discussion	446

7.3.5	Phase-Lock Velocity and Range Sensing with Ultrasound or EM Radiation	446
7.4	Measurement of Force and Torque	454
7.4.1	Load Cells for Force Measurement	454
7.4.2	Torque Measurements	458
7.5	Pressure Measurements	463
7.5.1	Introduction	463
7.5.2	High-Pressure Sensors	463
7.5.3	Low-Pressure Sensors	472
7.6	Introduction to Substance Detection and Measurement Using Photons.....	479
7.6.1	Introduction	479
7.6.2	Dispersive Spectrophotometry	482
7.6.3	Nondispersive Spectrophotometry	488
7.6.3.1	Use of Nondispersive Spectrophotometry to Quantify CO ₂ Gas in Air	494
7.6.3.2	Nondispersive Photoacoustic Spectrophotometry	494
7.6.4	Fourier Transform IR Spectrophotometry	495
7.6.5	Single- and Multiple-Bubble Sonoluminescence.....	501
7.6.5.1	Introduction	501
7.6.5.2	Single-Bubble Sonoluminescence	501
7.6.5.3	Multiple-Bubble Sonoluminescence	504
7.6.5.4	Summary	504
7.7	Other Means of Substance Detection	505
7.7.1	Mass Spectrometry	505
7.7.2	Gas Chromatography	510
7.7.3	Surface Plasmon Resonance	516
7.8	Temperature Measurements.....	522
7.8.1	Temperature Standards.....	522
7.8.2	Some Common Means of Temperature Measurement.....	523
7.8.2.1	Mechanical Temperature Sensors.....	523
7.8.2.2	Electrical and Electronic Temperature Sensors	527
7.9	Chapter Summary.....	537
	Problems.....	538
8.	Basic Electrical Measurements	545
8.1	Introduction	545
8.2	DC Voltage Measurements	545
8.2.1	Types of Electromechanical DC Voltmeters.....	547
8.2.2	Electronic DC Voltmeters	555
8.3	Measurement of Static Electric Fields and the Potential of Charged Surfaces.....	559
8.4	DC Measurements	568
8.4.1	Electromechanical DC Ammeters.....	570
8.4.2	Electronic DC Ammeters.....	571
8.4.2.1	Error Analysis of the Shunt Picoammeter	572
8.4.2.2	Error Analysis of the Feedback Picoammeter.....	574
8.4.3	Magneto-Optic Current Sensors.....	576
8.5	AC Voltage Measurements.....	576
8.5.1	Electromechanical AC Voltmeters.....	577
8.5.2	Analog Electronic AC Voltmeters.....	581

8.5.2.1	AC Amplifier–Rectifier AC Voltmeters	582
8.5.2.2	Peak-Reading Electronic AC Voltmeters	583
8.5.2.3	True RMS AC Voltmeter of the Feedback Type	586
8.5.2.4	True RMS AC Voltmeters Using the Direct Conversion Approach	588
8.5.3	Measurements of Amplifier Noise Voltages, Noise Factor, and Figure	588
8.6	AC Measurements	596
8.6.1	Electromechanical (Analog) AC Ammeters	597
8.6.2	Electronic and Magneto-Optical AC Ammeters	599
8.7	Magnetic Field Measurements	601
8.8	Phase Measurements	611
8.8.1	Analog Phase Measurements	613
8.8.2	Digital Phase Detectors	616
8.9	Measurements of Frequency and Period (Time)	618
8.10	Measurement of Resistance, Capacitance, and Inductance	624
8.10.1	Resistance Measurements	624
8.10.2	Capacitance Measurements	630
8.10.2.1	Q Meter Used for Capacitance Measurement	630
8.10.2.2	Capacitance Measurement by Q/V	634
8.10.3	Inductance Measurements	639
8.10.3.1	Voltmeter Method of Estimating Inductance	639
8.10.3.2	Use of the Q Meter to Measure Inductance and Q	640
8.11	Vector Impedance Meters	641
8.12	Chapter Summary	643
	Problems	643
9.	Digital Interfaces in Measurement Systems	651
9.1	Introduction	651
9.2	Sampling Theorem	652
9.3	Quantization Noise	655
9.4	Dithering	658
9.5	DACs	661
9.6	Hold Operation	665
9.7	ADCs	667
9.7.1	Successive-Approximation ADCs	667
9.7.2	Tracking or Servo ADCs	669
9.7.3	Dual-Slope Integrating ADCs	671
9.7.4	Flash (Parallel) ADCs	673
9.7.5	Dynamic Range, Floating Point ADCs	675
9.7.6	Delta–Sigma ADCs	676
9.7.7	Data Acquisition Cards for PCs	681
9.8	IEEE-488 Instrumentation Bus (GPIB)	682
9.8.1	Summary of the GPIB Bus Structure	682
9.8.2	GPIB Operation	684
9.9	Serial Data Communications Links	685
9.9.1	RS-232C and D Interfaces	686
9.9.2	TRS-422, RS-423, and RS-485 Interfaces	688

9.9.3	Universal Serial Bus.....	689
9.9.3.1	Introduction	689
9.9.3.2	How USB Works: An Overview	691
9.9.3.3	Summary	693
9.10	CAMAC (IEEE-583) Modular Instrumentation Standard and the VXI Modular Instrumentation Architecture	693
9.11	How Transmission Lines Affect the Transfer of Digital Data	696
9.11.1	Transmission Line Model	696
9.11.2	Reflections on an Improperly Terminated, Lossless Transmission Line	698
9.12	Data Transmission on Fiber-Optic Cables.....	703
9.12.1	FOC Basics	703
9.12.2	Semiconductor Sources and Detectors Used in FOC Data Transmission.....	711
9.12.3	FOC Systems.....	713
9.13	Virtual Instruments	714
9.13.1	Introduction	714
9.13.2	PXI Systems.....	716
9.13.3	Summary.....	716
9.14	Chapter Summary.....	717
	Problems.....	718
10.	Introduction to Digital Signal Conditioning in Instrumentation	725
10.1	Introduction	725
10.2	Digital Filters and the z-Transform.....	725
10.3	Some Simple DSP Algorithms.....	731
10.4	Discrete and Fast Fourier Transforms and Their Applications.....	740
10.4.1	Use of Data Windows to Improve Spectral Resolution	741
10.4.2	Use of the DFT to Characterize Random Signals and Noise.....	744
10.4.3	Fast Fourier Transform.....	747
10.5	Digital Routines for Interpolating Discrete Data	749
10.5.1	Estimating Missing Data at the Sampling Instants	752
10.6	Chapter Summary.....	754
	Problems.....	754
11.	Solid-State Chemical Microsensors and Wireless Instrumentation.....	757
11.1	Introduction	757
11.2	Chemical Microsensor Designs	758
11.2.1	Silicon-Based Chemical Microsensors.....	758
11.2.1.1	Schottky Diode-Based Microsensors.....	758
11.2.1.2	MOS ChemFET	759
11.2.2	Metal Oxide Gas Sensors.....	763
11.2.2.1	Taguchi Gas Sensors	763
11.2.2.2	Modern Metal Oxide Gas Sensors	764
11.2.2.3	CO ₂ Microsensor Based on Tin Oxide Doped with Copper Oxide.....	767
11.3	Electronic Noses.....	768
11.3.1	Introduction	768
11.3.2	Rationale for Artificial Noses.....	768

11.3.3	Sensors for E-Nose Applications	769
11.3.4	Feature Extraction in E-Noses.....	781
11.3.5	Some Commercially Available E-Noses	784
11.4	Radio ICs for Wireless Data Transmission.....	785
11.4.1	EM Spectrum.....	785
11.4.2	Some UHF Radio Chips.....	786
11.4.3	Antennas for Radio Chips	787
11.4.3.1	Introduction	787
11.4.3.2	Fractal Antennas	788
11.5	Wireless Patient Monitoring Systems	793
11.5.1	Introduction.....	793
11.5.2	RF Communications Protocols Used in WDX and WPM.....	794
11.5.3	Commercial WPM Systems.....	795
11.6	Power Sources for Wireless Sensors, Effectors, and WDX.....	796
11.7	Absorbable Electronic Circuit Implants.....	799
11.8	Chapter Summary.....	801
	Problems.....	802
12.	Introduction to Mechanical Microsensors	805
12.1	Introduction to Microelectromechanical Systems	805
12.1.1	Nanoelectromechanical Systems.....	805
12.2	MEM Accelerometer and Pressure Sensor ICs	806
12.2.1	MEM Linear Accelerometers.....	806
12.2.2	MEM Pressure Sensors	809
12.3	MEM Rate Gyros.....	810
12.3.1	Introduction.....	810
12.3.2	Oscillating Disk Rate Gyro.....	810
12.3.3	Vibrating Mass MEM Gyros.....	816
12.3.4	Quartz Tuning Fork MEM Rate Gyro	817
12.3.5	Applications of MEM Gyros.....	817
12.4	Cantilever-Like MEMS and NEMS and Their Applications	819
12.4.1	Introduction.....	819
12.4.2	Applications of Cantilever-Based MEMS Sensors	819
12.4.3	Design of Cantilever MEMS and NEMS	821
12.4.3.1	Cantilever Materials and Fabrication.....	821
12.4.3.2	Cantilever Readout Methods.....	821
12.4.3.3	Static MEM Cantilever Deflection Sensing with Piezoresistors	822
12.4.3.4	Cantilever Beam Resonance Frequency.....	824
12.4.3.5	Excitation of Mechanical Oscillation of MEM Cantilevers.....	825
12.4.3.6	Vibrations in a Beam Clamped at Both Ends.....	826
12.4.3.7	Vibrations in a Circularly Clamped Thin Plate	826
12.4.4	Quartz Tuning Fork Biosensor.....	827
12.4.5	Liquid Viscosity Measurement Using Piezoceramic Resonators	827
12.5	Chapter Summary.....	829
	Problems.....	829

Contents

13. Examples of the Design of Measurement Systems	835
13.1 Introduction	835
13.2 Self-Nulling, Microdegree Resolution Polarimeter to Measure Glucose in Bioreactors	835
13.3 Design of a System to Detect, Measure, and Locate Partial Discharges in High-Voltage Coaxial Power Cables	845
13.4 Design of a Closed-Loop, Constant-Phase, Pulsed Laser Ranging System and Velocimeter.....	852
13.5 Design of Capacitive Sensors for the Detection of Hidden Objects	858
13.5.1 Introduction.....	858
13.5.2 Self-Balancing Circuits Used to Measure $\Delta C/C_o$	860
13.5.3 Summary.....	864
13.6 Chapter Summary.....	864
Glossary	867
References	881
Index	899