

Contents

Preface ix

Section 1 Basic Electrical and Electronic Engineering Principles 1

1	Units associated with basic electrical quantities	3
1.1	SI units	3
1.2	Charge	4
1.3	Force	4
1.4	Work	4
1.5	Power	4
1.6	Electrical potential and e.m.f.	5
1.7	Resistance and conductance	6
1.8	Electrical power and energy	6
1.9	Summary of terms, units and their symbols	7
2	An introduction to electric circuits	9
2.1	Electrical/electronic system block diagrams	10
2.2	Standard symbols for electrical components	11
2.3	Electric current and quantity of electricity	11
2.4	Potential difference and resistance	12
2.5	Basic electrical measuring instruments	12
2.6	Linear and non-linear devices	13
2.7	Ohm's law	13
2.8	Multiples and sub-multiples	13
2.9	Conductors and insulators	15
2.10	Electrical power and energy	15
2.11	Main effects of electric current	18
2.12	Fuses	18
2.13	Insulation and the dangers of constant high current flow	19
3	Resistance variation	21
3.1	Resistor construction	21
3.2	Resistance and resistivity	22
3.3	Temperature coefficient of resistance	24
3.4	Resistor colour coding and ohmic values	26
4	Batteries and alternative sources of energy	30
4.1	Introduction to batteries	31
4.2	Some chemical effects of electricity	31
4.3	The simple cell	32

4.4	Corrosion	33
4.5	E.m.f. and internal resistance of a cell	33
4.6	Primary cells	36
4.7	Secondary cells	36
4.8	Cell capacity	37
4.9	Safe disposal of batteries	39
4.10	Fuel cells	39
4.11	Alternative and renewable energy sources	39

Revision Test 1 43

5	Series and parallel networks	44
5.1	Series circuits	44
5.2	Potential divider	46
5.3	Parallel networks	47
5.4	Current division	50
5.5	Loading effect	54
5.6	Potentiometers and rheostats	55
5.7	Relative and absolute voltages	57
5.8	Earth potential and short circuits	59
5.9	Wiring lamps in series and in parallel	59
6	Capacitors and capacitance	62
6.1	Introduction to capacitors	63
6.2	Electrostatic field	63
6.3	Electric field strength	64
6.4	Capacitance	64
6.5	Capacitors	64
6.6	Electric flux density	66
6.7	Permittivity	66
6.8	The parallel plate capacitor	67
6.9	Capacitors connected in parallel and series	69
6.10	Dielectric strength	73
6.11	Energy stored in capacitors	73
6.12	Practical types of capacitor	74
6.13	Supercapacitors	76
6.14	Discharging capacitors	77
7	Magnetic circuits	80
7.1	Introduction to magnetism and magnetic circuits	81
7.2	Magnetic fields	81
7.3	Magnetic flux and flux density	82
7.4	Magnetomotive force and magnetic field strength	82
7.5	Permeability and B-H curves	83

7.6 Reluctance	86	11 Semiconductor diodes	148
7.7 Composite series magnetic circuits	87	11.1 Types of material	149
7.8 Comparison between electrical and magnetic quantities	90	11.2 Semiconductor materials	149
7.9 Hysteresis and hysteresis loss	90	11.3 Conduction in semiconductor materials	151
		11.4 The p-n junction	151
		11.5 Forward and reverse bias	152
Revision Test 2	93	11.6 Semiconductor diodes	155
8 Electromagnetism	94	11.7 Characteristics and maximum ratings	156
8.1 Magnetic field due to an electric current	95	11.8 Rectification	156
8.2 Electromagnets	96	11.9 Zener diodes	156
8.3 Force on a current-carrying conductor	98	11.10 Silicon controlled rectifiers	158
8.4 Principle of operation of a simple d.c. motor	101	11.11 Light emitting diodes	158
8.5 Principle of operation of a moving-coil instrument	101	11.12 Varactor diodes	159
8.6 Force on a charge	102	11.13 Schottky diodes	159
9 Electromagnetic induction	105	12 Transistors	163
9.1 Introduction to electromagnetic induction	106	12.1 Transistor classification	164
9.2 Laws of electromagnetic induction	106	12.2 Bipolar junction transistors (BJTs)	164
9.3 Rotation of a loop in a magnetic field	109	12.3 Transistor action	165
9.4 Inductance	110	12.4 Leakage current	166
9.5 Inductors	112	12.5 Bias and current flow	166
9.6 Energy stored	112	12.6 Transistor operating configurations	167
9.7 Inductance of a coil	113	12.7 Bipolar transistor characteristics	167
9.8 Mutual inductance	115	12.8 Transistor parameters	169
10 Electrical measuring instruments and measurements	119	12.9 Current gain	171
10.1 Introduction	120	12.10 Typical BJT characteristics and maximum ratings	171
10.2 Analogue instruments	120	12.11 Field effect transistors	172
10.3 Moving-iron instrument	120	12.12 Field effect transistor characteristics	173
10.4 The moving-coil rectifier instrument	121	12.13 Typical FET characteristics and maximum ratings	175
10.5 Comparison of moving-coil, moving-iron and moving-coil rectifier instruments	121	12.14 Transistor amplifiers	175
10.6 Shunts and multipliers	121	12.15 Load lines	177
10.7 Electronic instruments	123		
10.8 The ohmmeter	124	Revision Test 3	184
10.9 Multimeters	124		
10.10 Wattmeters	124	Formulae for basic electrical and electronic principles	185
10.11 Instrument 'loading' effect	125		
10.12 The oscilloscope	127	Section 2 Further Electrical and Electronic Principles	187
10.13 Virtual test and measuring instruments	131		
10.14 Virtual digital storage oscilloscopes	132	13 D.c. circuit theory	189
10.15 Waveform harmonics	135	13.1 Introduction	189
10.16 Logarithmic ratios	136	13.2 Kirchhoff's laws	190
10.17 Null method of measurement	139	13.3 The superposition theorem	193
10.18 Wheatstone bridge	139	13.4 General d.c. circuit theory	196
10.19 D.c. potentiometer	140	13.5 Thévenin's theorem	198
10.20 A.c. bridges	141	13.6 Constant-current source	203
10.21 Q-meter	142	13.7 Norton's theorem	203
10.22 Measurement errors	143		

13.8	Thévenin and Norton equivalent networks	207	18.7	Current growth in an $L-R$ circuit	293
13.9	Maximum power transfer theorem	210	18.8	Time constant for an $L-R$ circuit	294
14	Alternating voltages and currents	215	18.9	Transient curves for an $L-R$ circuit	294
14.1	Introduction	216	18.10	Current decay in an $L-R$ circuit	296
14.2	The a.c. generator	216	18.11	Switching inductive circuits	298
14.3	Waveforms	217	18.12	The effects of time constant on a rectangular waveform	298
14.4	A.c. values	218	19	Operational amplifiers	302
14.5	Electrical safety – insulation and fuses	221	19.1	Introduction to operational amplifiers	303
14.6	The equation of a sinusoidal waveform	222	19.2	Some op amp parameters	304
14.7	Combination of waveforms	224	19.3	Op amp inverting amplifier	305
14.8	Rectification	227	19.4	Op amp non-inverting amplifier	308
14.9	Smoothing of the rectified output waveform	228	19.5	Op amp voltage-follower	308
			19.6	Op amp summing amplifier	309
			19.7	Op amp voltage comparator	310
			19.8	Op amp integrator	311
			19.9	Op amp differential amplifier	311
			19.10	Digital to analogue (D/A) conversion	313
			19.11	Analogue to digital (A/D) conversion	315
Revision Test 4		232	Revision Test 5		318
15	Single-phase series a.c. circuits	233	Formulae for further electrical and electronic principles		319
15.1	Purely resistive a.c. circuit	234	Section 3	Electrical Power Technology	321
15.2	Purely inductive a.c. circuit	234	20	Three-phase systems	323
15.3	Purely capacitive a.c. circuit	235	20.1	Introduction	324
15.4	$R-L$ series a.c. circuit	236	20.2	Three-phase supply	324
15.5	$R-C$ series a.c. circuit	240	20.3	Star connection	324
15.6	$R-L-C$ series a.c. circuit	241	20.4	Delta connection	328
15.7	Series resonance	245	20.5	Power in three-phase systems	329
15.8	Q-factor	246	20.6	Measurement of power in three-phase systems	331
15.9	Bandwidth and selectivity	247	20.7	Comparison of star and delta connections	336
15.10	Power in a.c. circuits	248	20.8	Advantages of three-phase systems	336
15.11	Power triangle and power factor	249	21	Transformers	339
16	Single-phase parallel a.c. circuits	254	21.1	Introduction	340
16.1	Introduction	255	21.2	Transformer principle of operation	340
16.2	$R-L$ parallel a.c. circuit	255	21.3	Transformer no-load phasor diagram	342
16.3	$R-C$ parallel a.c. circuit	256	21.4	E.m.f. equation of a transformer	344
16.4	$L-C$ parallel circuit	257	21.5	Transformer on-load phasor diagram	346
16.5	$LR-C$ parallel a.c. circuit	259	21.6	Transformer construction	347
16.6	Parallel resonance and Q-factor	262	21.7	Equivalent circuit of a transformer	348
16.7	Power factor improvement	266	21.8	Regulation of a transformer	350
17	Filter networks	273	21.9	Transformer losses and efficiency	350
17.1	Introduction	273	21.10	Resistance matching	353
17.2	Two-port networks and characteristic impedance	274	21.11	Auto transformers	355
17.3	Low-pass filters	274	21.12	Isolating transformers	357
17.4	High-pass filters	277	21.13	Three-phase transformers	357
17.5	Band-pass filters	281			
17.6	Band-stop filters	282			
18	D.c. transients	285			
18.1	Introduction	286			
18.2	Charging a capacitor	286			
18.3	Time constant for a $C-R$ circuit	287			
18.4	Transient curves for a $C-R$ circuit	287			
18.5	Discharging a capacitor	291			
18.6	Camera flash	293			

21.14	Current transformers	359	23.10	Induction motor losses and efficiency	397
21.15	Voltage transformers	360	23.11	Torque equation for an induction motor	398
Revision Test 6		363	23.12	Induction motor torque–speed characteristics	401
22	D.c. machines	364	23.13	Starting methods for induction motors	402
22.1	Introduction	365	23.14	Advantages of squirrel-cage induction motors	402
22.2	The action of a commutator	365	23.15	Advantages of wound rotor induction motors	403
22.3	D.c. machine construction	366	23.16	Double cage induction motor	403
22.4	Shunt, series and compound windings	366	23.17	Uses of three-phase induction motors	404
22.5	E.m.f. generated in an armature winding	367	Revision Test 7		407
22.6	D.c. generators	369	Formulae for electrical power technology		408
22.7	Types of d.c. generator and their characteristics	369	Section 4 Laboratory Experiments		409
22.8	D.c. machine losses	373	24	Some practical laboratory experiments	411
22.9	Efficiency of a d.c. generator	373	24.1	Ohm's law	412
22.10	D.c. motors	374	24.2	Series–parallel d.c. circuit	413
22.11	Torque of a d.c. motor	375	24.3	Superposition theorem	414
22.12	Types of d.c. motor and their characteristics	377	24.4	Thévenin's theorem	416
22.13	The efficiency of a d.c. motor	380	24.5	Use of a CRO to measure voltage, frequency and phase	418
22.14	D.c. motor starter	383	24.6	Use of a CRO with a bridge rectifier	419
22.15	Speed control of d.c. motors	383	24.7	Measurement of the inductance of a coil	420
22.16	Motor cooling	386	24.8	Series a.c. circuit and resonance	421
23	Three-phase induction motors	389	24.9	Parallel a.c. circuit and resonance	423
23.1	Introduction	390	24.10	Charging and discharging a capacitor	425
23.2	Production of a rotating magnetic field	390	Answers to Practice Exercises		426
23.3	Synchronous speed	392	Index		439
23.4	Construction of a three-phase induction motor	393			
23.5	Principle of operation of a three-phase induction motor	393			
23.6	Slip	394			
23.7	Rotor e.m.f. and frequency	395			
23.8	Rotor impedance and current	396			
23.9	Rotor copper loss	396			