

# Contents

<b>Preface</b>	<i>xi</i>
<b>List of Abbreviations</b>	<i>xvii</i>
<b>List of Symbols</b>	<i>xix</i>

<b>1</b>	<b>Introduction to Power System Analysis</b>	<i>1</i>
1.1	Introduction	<i>1</i>
1.2	Scope of the Material	<i>2</i>
1.3	General Characteristics of Power Systems	<i>5</i>
1.3.1	AC versus DC Systems	<i>5</i>
	Shape of the alternating voltage	<i>6</i>
	Sinusoidal alternating voltage	<i>7</i>
1.3.2	50 and 60 Hz Frequency	<i>9</i>
1.3.3	Balanced Three-Phase Systems	<i>10</i>
	Power considerations	<i>12</i>
	Rotating magnetic field	<i>14</i>
1.3.4	Voltage Levels	<i>17</i>
	Line-to-line and line-to-neutral voltages	<i>19</i>
1.4	Phasors	<i>20</i>
1.4.1	Network Elements in the Phasor Domain	<i>22</i>
1.4.2	Calculations in the Phasor Domain	<i>24</i>
1.5	Equivalent Line-to-neutral Diagrams	<i>28</i>
1.6	Power in Single-phase Circuits	<i>30</i>
1.6.1	Active and Reactive Power	<i>31</i>
1.6.2	Complex Power	<i>34</i>
1.6.3	Power Factor	<i>38</i>
1.7	Power in Three-phase Circuits	<i>40</i>
1.8	Per-unit Normalization	<i>41</i>
1.9	Power System Structure	<i>45</i>
	Problems	<i>47</i>
	References	<i>49</i>

<b>2</b>	<b>The Generation of Electric Energy</b>	<b>51</b>
2.1	Introduction	51
2.2	Thermal Power Plants	53
2.2.1	The Principles of Thermodynamics	53
2.3	Nuclear Power Plants	58
2.3.1	Nuclear Fission	59
2.3.2	Nuclear Fusion	62
2.4	Renewable Energy	63
2.4.1	Wind Energy and Wind Turbine Concepts	63
2.4.2	Hydropower and Pumped Storage	67
2.4.3	Solar Power	69
2.4.4	Geothermal Power	71
2.5	The Synchronous Machine	74
	Problems	82
	References	84
<b>3</b>	<b>The Transmission of Electric Energy</b>	<b>85</b>
3.1	Introduction	85
3.2	Transmission and Distribution Network	86
3.3	Network Structures	89
3.4	Substations	91
3.5	Substation Concepts	93
3.5.1	Single Bus System	94
3.5.2	Double Bus System	95
3.5.3	Polygon Bus System	96
3.5.4	One-and-a-Half Circuit Breaker Concept	96
3.6	Protection of Transmission and Distribution Networks	97
3.6.1	Protective Relay Operating Principles	99
3.6.2	Fuses	104
3.6.3	Circuit Breakers	106
3.6.4	The Switching Arc	107
3.6.5	Oil Circuit Breakers	109
3.6.6	Air-Blast Circuit Breakers	109
3.6.7	SF <sub>6</sub> Circuit Breakers	110
3.6.8	Vacuum Circuit Breakers	112
3.7	Surge Arresters	113
3.8	Transformers	115
3.8.1	Phase Shifts in Three-Phase Transformers	119
3.8.2	The Magnetizing Current	123
3.8.3	Transformer Inrush Current	126
3.8.4	Open Circuit and Short Circuit Tests	127

- 3.9 Power Carriers 129
- 3.9.1 Overhead Transmission Lines 131
  - Insulators 131
  - Bundled conductors 134
  - Galloping lines 138
  - Ground wires or shield wires 141
  - Transposition 144
- 3.9.2 Underground Cables 145
  - Plastic insulation 147
  - Paper–oil insulation 148
- 3.9.3 Gas-Insulated Transmission Lines 151
- 3.10 High-Voltage Direct Current Transmission 152
  - From AC to DC 156
  - Problems 160
  - References 161

#### **4 The Utilization of Electric Energy 163**

- 4.1 Introduction 163
- 4.2 Types of Load 164
  - 4.2.1 Mechanical Energy 165
    - Synchronous motors 166
    - Induction motors 168
  - 4.2.2 Light 171
  - 4.2.3 Heat 173
  - 4.2.4 DC Electrical Energy 173
  - 4.2.5 Chemical Energy 175
- 4.3 Classification of Grid Users 177
  - 4.3.1 Residential Loads 177
  - 4.3.2 Commercial and Industrial Loads 179
  - 4.3.3 Electric Railways 180
    - Problems 182
    - Reference 184

#### **5 Power System Control 185**

- 5.1 Introduction 185
- 5.2 Basics of Power System Control 187
- 5.3 Active Power and Frequency Control 190
  - 5.3.1 Primary Control 190
  - 5.3.2 Secondary Control or Load Frequency Control (LFC) 196

5.4	Voltage Control and Reactive Power	198
5.4.1	Generator Control (AVR)	199
5.4.2	Tap-Changing Transformers	201
5.4.3	Reactive Power Injection	203
	Static shunt capacitors and reactors	203
	Synchronous compensators	204
	Static var compensator (SVC)	204
	Static synchronous compensator (STATCOM)	206
5.5	Control of Transported Power	207
5.5.1	Controlling Active Power Flows	207
	The phase shifter	208
5.5.2	Controlling Reactive Power Flows	210
	Static series capacitors	211
	Thyristor-controlled series capacitor (TCSC)	211
	Static synchronous series compensator (SSSC)	212
5.5.3	Unified Power Flow Controller (UPFC)	214
5.6	Flexible AC Transmission Systems (FACTS)	215
	Problems	215
	References	218
<b>6</b>	<b>Energy Management Systems</b>	<b>219</b>
6.1	Introduction	219
6.2	Load Flow or Power Flow Computation	220
6.2.1	Load Flow Equations	220
6.2.2	General Scheme of the Newton–Raphson Load Flow	230
6.2.3	Decoupled Load Flow	234
6.2.4	DC Load Flow	238
	Active power equations	239
	Reactive power equations	240
6.3	Optimal Power Flow	241
6.4	State Estimator	242
6.4.1	General Scheme of the State Estimator	245
6.4.2	Bad Data Analysis	247
6.4.3	Statistical Analysis of the State Estimator	254
	Properties of the estimates	254
	Bad data detection	255
	Bad data identification	256
	Problems	257
	References	260
<b>7</b>	<b>Electricity Markets</b>	<b>261</b>
7.1	Introduction	261
7.2	Electricity Market Structure	262

- 7.2.1 Transmission and Distribution 262
- 7.2.2 Market Architecture 263
- 7.3 Market Clearing 265
- 7.4 Social Welfare 267
- 7.5 Market Coupling 269
- 7.6 Allocation Mechanism and Zonal/Nodal Markets 274
- References 277

**8 Future Power Systems 279**

- 8.1 Introduction 279
- 8.2 Renewable Energy 280
- 8.3 Decentralized or Distributed Generation 281
- 8.4 Power-Electronic Interfaces 285
- 8.5 Energy Storage 286
- 8.6 Blackouts and Chaotic Phenomena 287
- 8.6.1 Nonlinear Phenomena and Chaos 287
- 8.6.2 Blackouts 290
- References 298

**A Maxwell's Laws 299**

- A.1 Introduction 299
- A.2 Power Series Approach to Time-Varying Fields 300
- A.3 Quasi-static Field of a Parallel-plate Capacitor 302
- A.3.1 Quasi-static Solution 303
- A.3.2 Validity of the Quasi-static Approach 305
- A.4 Quasi-static Field of a Single-turn Inductor 307
- A.4.1 Quasi-static Solution 308
- A.4.2 Validity of the Quasi-static Approach 310
- A.5 Quasi-static Field of a Resistor 312
- A.5.1 Quasi-static Solution 312
- A.6 Circuit Modeling 315
- Reference 316

**B Power Transformer Model 317**

- B.1 Introduction 317
- B.2 The Ideal Transformer 317
- B.3 Magnetically Coupled Coils 320
- B.3.1 Equivalence with the Ideal Transformer 323
- B.4 The Nonideal Transformer 324
- B.5 Three-Phase Transformer 327

**C Synchronous Machine Model 329**

- C.1 Introduction 329
- C.2 The Primitive Synchronous Machine 329

- C.3 The Single-Phase Synchronous Machine 335
- C.4 The Three-Phase Synchronous Machine 341
- C.5 Synchronous Generator in the Power System 345

**D Induction Machine Model 349**

- D.1 Introduction 349
- D.2 The Basic Principle of the Induction Machine 350
  - D.2.1 A Single Rotor Winding 351
  - D.2.2 Two Rotor Windings 354
  - D.2.3 Rotating Rotor 354
- D.3 The Magnetic Field in the Air Gap 356
  - D.3.1 Contribution of the Rotor Currents to the Air-Gap Field 356
  - D.3.2 The Flux Linkage with the Stator Windings 359
- D.4 A Simple Circuit Model for the Induction Machine 360
  - D.4.1 The Stator Voltage Equation 360
  - D.4.2 The Induction Machine as Two Magnetically Coupled Coils 361
  - D.4.3 A Practical Model of the Induction Machine 362
- D.5 Induction Motor in the Power System 363

**E The Representation of Lines and Cables 365**

- E.1 Introduction 365
- E.2 The Long Transmission Line 365
- E.3 The Medium-Length Transmission Line 370
- E.4 The Short Transmission Line 371
- E.5 Comparison of the Three Line Models 371
- E.6 The Underground Cable 374

**Solutions 375**

**Further Reading 391**

**Index 393**