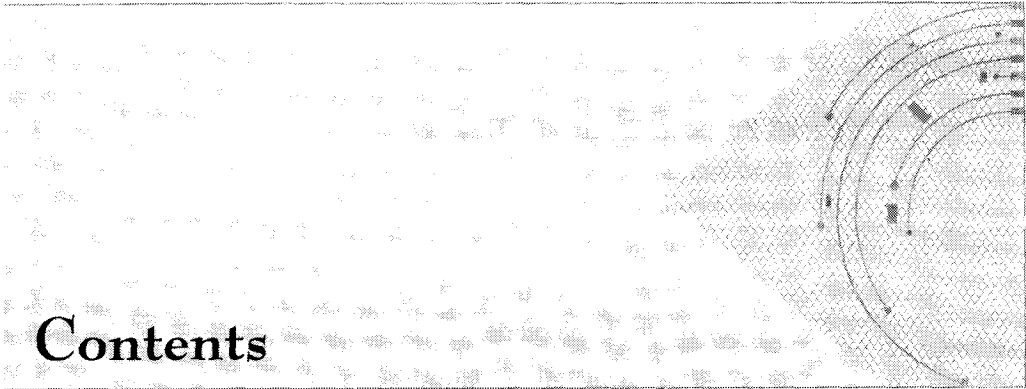




Contents

Preface

v

1. Physical Properties of Elements	1.1
1.1 Introduction	1.1
1.2 Atomic Structure	1.1
1.3 Bohr's Atomic Model	1.2
1.4 Atomic Energy Level Diagram	1.5
1.5 Electronic Configuration of Elements	1.6
1.6 Energy Band Theory of Solids	1.9
1.7 Classification of Solids on the Basis of Energy Bands	1.12
1.8 Commonly used Semiconductor Materials	1.15
2. Semiconductor Diodes	2.1
2.1 Introduction	2.1
2.2 Theory of <i>P-N</i> -Junction Diode	2.3
2.3 Limitations in the Operating Conditions of <i>P-N</i> -Junction	2.15
2.4 Diode Current Equation	2.16
2.5 Effect of Temperature on <i>P-N</i> -Junction Diode Characteristics	2.20
2.6 Breakdown in <i>P-N</i> -Junction Diode	2.21
2.7 Diode Resistance	2.22
2.8 Space Charge Capacitance or Transition Capacitance (C_T)	2.26
2.9 Diffusion Capacitance (C_D)	2.32
2.10 Zener Diode	2.32
2.11 Diode Clippers	2.34
2.12 Diode Clamper	2.37

3. Special Purpose Electronic Devices	3.1
3.1 Introduction	3.1
3.2 Tunnel Diode	3.1
3.3 Varactor Diode	3.6
3.4 Silicon Controlled Rectifier (SCR)	3.9
3.5 Semiconductor Photodiode	3.14
4. Rectifiers, Filters and Power Supplies	4.1
4.1 Introduction	4.1
4.2 Rectifiers	4.1
4.3 Filter Circuits	4.19
4.4 Power Supply	4.24
4.5 Zener Diode as a Voltage Regulator	4.24
5. Bipolar Junction Transistor	5.1
5.1 Introduction	5.1
5.2 Transistor	5.1
5.3 Transistor Terminals	5.2
5.4 Modes of Operation	5.3
5.5 Operation of $P-N-P$ Transistor	5.3
5.6 Operation of $N-P-N$ Transistor	5.4
5.7 Transistor Current Components	5.4
5.8 Transistor Circuit Configurations	5.5
5.9 Common Base Configuration	5.6
5.10 Common Emitter Configuration	5.8
5.11 Characteristics of Common-emitter Configuration	5.13
5.12 Common Collector Configuration	5.15
5.13 Comparative Study of CB, CE and CC Configurations	5.16
5.14 Transistor as an Amplifier	5.17
6. Transistor Biasing and Stabilization	6.1
6.1 Introduction	6.1
6.2 Location of the Operating Point: The Load Line	6.1
6.3 Operating Point or Quiescent Point	6.2
6.4 Need for Biasing	6.5
6.5 Thermal Runaway	6.6
6.6 Stability Factor	6.6
6.7 Different Biasing Circuits	6.6
6.8 Bias Stability	6.19

6.9	Stabilisation Against Variation in V_{BE} , and β	6.19
6.10	BIAS Compensation	6.20
7.	Hybrid Parameters and UJT	7.1
7.1	Introduction	7.1
7.2	The Hybrid Equivalent Model	7.1
7.3	Hybrid Model	7.3
7.4	Determination of h -Parameters from Transistor Characteristics	7.5
7.5	Performance of Linear Circuit in h -Parameters	7.7
7.6	Transistor Circuit Performance in h -Parameters	7.10
7.7	Comparison of Three Types of Amplifier Circuits	7.11
7.8	Unijunction Transistor (UJT)	7.12
7.9	UJT Parameters	7.12
7.10	Operation of UJT	7.13
7.11	Characteristics of UJT	7.14
8.	Field Effect Transistors	8.1
8.1	Introduction	8.1
8.2	Field Effect Transistor (FET)	8.1
8.3	Construction of JFET	8.1
8.4	Operation of JFET	8.4
8.5	Volt-Ampere Characteristics of JFET	8.5
8.6	JFET Parameters	8.9
8.7	Relation Between μ , r_d and g_m	8.10
8.8	Mathematical Expression for g_m	8.11
8.9	The FET Small Signal Model	8.12
8.10	Merits and Demerits of JFET	8.14
8.11	Application of JFET	8.14
8.12	Metal Oxide Semiconductor Field Effect Transistor (MOSFET)	8.15
8.13	Construction of Depletion Type MOSFET	8.15
8.14	Working of Depletion Type MOSFET	8.16
8.15	Characteristics of Depletion Type MOSFET	8.17
8.16	Construction of Enhancement Type MOSFET	8.18
8.17	Working of Enhancement Type MOSFET	8.19
8.18	Characteristics of Enhancement Type MOSFET	8.20
8.19	Advantages of N -channel MOSFETs over P -channel	8.22

8.20	Comparison Between the JFET and MOSFET	8.22
8.21	Applications of MOSFET	8.23
9.	FET Amplifiers	9.1
9.1	Introduction	9.1
9.2	Biasing the JFET	9.1
9.3	Field Effect Transistor Amplifier	9.5
9.4	Fet as a Voltage Variable Resistor (VVR)	9.13
9.5	Comparison Between Field Effect Transistor and Bipolar Junction Transistor	9.14
<i>Index</i>		<i>1.1-1.8</i>