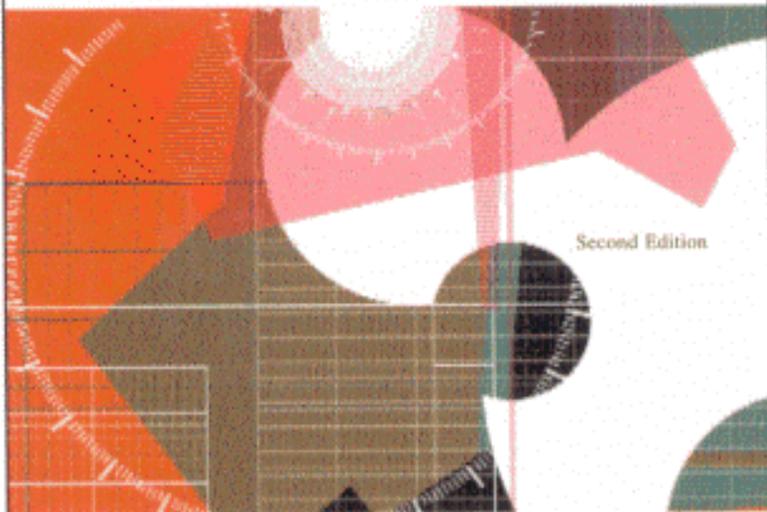


INTERNATIONAL EDITION



*Introduction to*  
**MECHATRONICS**  
*and Measurement Systems*



Second Edition

David G. Alciatore  Michael B. Hstand

**M c G R A W - H I L L**

## Lists ix

Figures ix

Tables xiv

Class Discussion Items xv

Examples xvii

Design Examples xviii

## Preface xix

### Chapter 1

## Introduction to Mechatronics and Measurement Systems 1

1.1 Mechatronics 1

1.2 Measurement Systems 4

### Chapter 2

## Electric Circuits and Components 6

2.1 Introduction 7

2.2 Basic Electrical Elements 9

2.2.1 Resistor 10

2.2.2 Capacitor 13

2.2.3 Inductor 14

2.3 Kirchhoff's Laws 16

2.3.1 Series Resistance Circuit 18

2.3.2 Parallel Resistance Circuit 20

2.4 Voltage and Current Sources and Meters 23

2.5 Thevenin and Norton Equivalent Circuits 29

2.6 Alternating Current Circuit Analysis 30

2.7 Power in Electrical Circuits 36

2.8 Transformer 38

2.9 Impedance Matching 39

2.10 Grounding and Electrical Interference 41

2.10.1 Electrical Safety 44

### Chapter 3

## Semiconductor Electronics 53

3.1 Introduction 54

3.2 Semiconductor Physics as the Basis for Understanding Electronic Devices 54

3.3 Junction Diode 56

3.3.1 Zener Diode 60

3.3.2 Voltage Regulators 65

3.3.3 Optoelectronic Diodes 66

3.3.4 Analysis of Diode Circuits 67

3.4 Bipolar Junction Transistor 70

3.4.1 Bipolar Transistor Physics 70

3.4.2 Common Emitter Transistor Circuit 72

3.4.3 Bipolar Transistor Switch 74

3.4.4 Bipolar Transistor Packages 77

3.4.5 Darlington Transistor 77

3.4.6 Phototransistor and Opto-Isolator 78

3.5 Field Effect Transistors 80

3.5.1 Behavior of Field-Effect Transistors 81

3.5.2 Symbols Representing Field Effect Transistors 83

3.5.3 Applications of MOSFETs 84

### Chapter 4

## System Response 96

4.1 System Response 97

4.2 Amplitude Linearity 98

4.3 Fourier Series Representation of Signals 99

4.4 Bandwidth and Frequency Response 102

- 4.5 Phase Linearity 108
- 4.6 Distortion of Signals 109
- 4.7 Dynamic Characteristics of Systems 110
- 4.8 Zero-Order System 111
- 4.9 First-Order System 112
  - 4.9.1 *Experimental Testing of a First-Order System* 114
- 4.10 Second-Order System 115
  - 4.10.1 *Step Response of a Second-Order System* 119
  - 4.10.2 *Frequency Response of a System* 121
- 4.11 System Modeling and Analogies 130

## Chapter 5

### **Analog Signal Processing Using Operational Amplifiers** 141

- 5.1 Introduction 142
- 5.2 Amplifiers 142
- 5.3 Operational Amplifiers 144
- 5.4 Ideal Model for the Operational Amplifier 144
- 5.5 Inverting Amplifier 147
- 5.6 Noninverting Amplifier 150
- 5.7 Summer 152
- 5.8 Difference Amplifier 152
- 5.9 Instrumentation Amplifier 155
- 5.10 Integrator 157
- 5.11 Differentiator 158
- 5.12 Sample and Hold Circuit 159
- 5.13 Comparator 160
- 5.14 The Real Op Amp 161
  - 5.14.1 *Important Parameters from Op Amp Data Sheets* 163

## Chapter 6

### **Digital Circuits** 178

- 6.1 Introduction 179
- 6.2 Digital Representations 180
- 6.3 Combinational Logic and Logic Classes 183
- 6.4 Timing Diagrams 186

- 6.5 Boolean Algebra 187
- 6.6 Design of Logic Networks 189
  - 6.6.1 *Define the Problem in Words* 189
  - 6.6.2 *Write Quasi-Logic Statements* 190
  - 6.6.3 *Write the Boolean Expression* 190
  - 6.6.4 *AND Realization* 191
  - 6.6.5 *Draw the Circuit Diagram* 191
- 6.7 Finding a Boolean Expression Given a Truth Table 192
- 6.8 Sequential Logic 194
- 6.9 Flip-Flops 195
  - 6.9.1 *Triggering of Flip-Flops* 196
  - 6.9.2 *Asynchronous Inputs* 198
  - 6.9.3 *D Flip-Flop* 199
  - 6.9.4 *JK Flip-Flop* 200
- 6.10 Applications of Flip-Flops 203
  - 6.10.1 *Switch Debouncing* 203
  - 6.10.2 *Data Register* 204
  - 6.10.3 *Binary Counter and Frequency Divider* 205
  - 6.10.4 *Serial and Parallel Interfaces* 205
- 6.11 TTL and CMOS Integrated Circuits 207
  - 6.11.1 *Using Manufacturer IC Data Sheets* 209
  - 6.11.2 *Digital IC Output Configurations* 213
  - 6.11.3 *Interfacing TTL and CMOS Devices* 215
- 6.12 Special Purpose Digital Integrated Circuits 217
  - 6.12.1 *Decade Counter* 217
  - 6.12.2 *Schmitt Trigger* 220
  - 6.12.3 *555 Timer* 220
- 6.13 Integrated Circuit System Design 224
  - 6.13.1 *IEEE Standard Digital Symbols* 227

## Chapter 7

### **Microcontroller Programming and Interfacing** 238

- 7.1 Microprocessors and Microcomputers 239
- 7.2 Microcontrollers 242
- 7.3 The PIC16F84 Microcontroller 244
- 7.4 Programming a PIC 248

- 7.5 PicBasic Pro** 254
  - 7.5.1 *PicBasic Pro Programming Fundamentals* 254
  - 7.5.2 *PicBasic Pro Programming Examples* 262
- 7.6 Using Interrupts** 274
- 7.7 Interfacing Common PIC Peripherals** 277
  - 7.7.1 *Numeric Keypad* 278
  - 7.7.2 *LCD Display* 280
- 7.8 Interfacing to the PIC** 282
  - 7.8.1 *Digital Input to the PIC* 284
  - 7.8.2 *Digital Output from the PIC* 287
- 7.9 Method to Design a Microcontroller-Based System** 287

## Chapter 8

### **Data Acquisition** 297

- 8.1 Introduction** 298
- 8.2 Quantizing Theory** 302
- 8.3 Analog-to-Digital Conversion** 303
  - 8.3.1 *Introduction* 303
  - 8.3.2 *Analog-to-Digital Converters* 307
- 8.4 Digital-to-Analog (D/A) Conversion** 310

## Chapter 9

### **Sensors** 315

- 9.1 Introduction** 316
- 9.2 Position and Speed Measurement** 316
  - 9.2.1 *Proximity Sensors and Switches* 317
  - 9.2.2 *Potentiometer* 318
  - 9.2.3 *Linear Variable Differential Transformer* 319
  - 9.2.4 *Digital Optical Encoder* 322
- 9.3 Stress and Strain Measurement** 330
  - 9.3.1 *Electrical Resistance Strain Gage* 330
  - 9.3.2 *Measuring Resistance Changes with a Wheatstone Bridge* 335
  - 9.3.3 *Measuring Different States of Stress with Strain Gages* 339
  - 9.3.4 *Force Measurement with Load Cells* 345

- 9.4 Temperature Measurement** 347
  - 9.4.1 *Liquid-in-Glass Thermometer* 348
  - 9.4.2 *Bimetallic Strip* 348
  - 9.4.3 *Electrical Resistance Thermometer* 349
  - 9.4.4 *Thermocouple* 349
- 9.5 Vibration and Acceleration Measurement** 357
  - 9.5.1 *Piezoelectric Accelerometer* 362
- 9.6 Pressure and Flow Measurement** 366
- 9.7 Semiconductor Sensors and Microelectromechanical Devices** 366

## Chapter 10

### **Actuators** 372

- 10.1 Introduction** 373
- 10.2 Electromagnetic Principles** 373
- 10.3 Solenoids and Relays** 374
- 10.4 Electric Motors** 376
- 10.5 DC Motors** 383
  - 10.5.1 *DC Motor Electrical Equations* 386
  - 10.5.2 *Permanent Magnet DC Motor Dynamic Equations* 386
  - 10.5.3 *Electronic Control of a Permanent Magnet DC Motor* 389
- 10.6 Stepper Motors** 393
  - 10.6.1 *Stepper Motor Drive Circuits* 397
- 10.7 Selecting a Motor** 400
- 10.8 Hydraulics** 404
  - 10.8.1 *Hydraulic Valves* 406
  - 10.8.2 *Hydraulic Actuators* 410
- 10.9 Pneumatics** 411

## Chapter 11

### **Mechatronic Systems—Control Architectures and Case Studies** 416

- 11.1 Introduction** 417
- 11.2 Control Architectures** 417
  - 11.2.1 *Analog Circuits* 417
  - 11.2.2 *Digital Circuits* 418

- 11.2.3 Programmable Logic Controller 418
  - 11.2.4 Microcontroller 418
  - 11.2.5 Single-Board Computer 418
  - 11.2.6 Personal Computer 419
  - 11.3 Case Study 1—Mechatronic Design of a Coin Counter 419
  - 11.4 Case Study 2—Mechatronic Design of a Robotic Walking Machine 429
  - 11.5 List of Various Mechatronic Systems 435
- Appendix A
- Measurement Fundamentals** 437
- A.1 Systems of Units 437
    - A.1.1 Three Classes of SI Units 439
    - A.1.2 Conversion Factors 441
  - A.2 Significant Figures 442
  - A.3 Statistics 444
  - A.4 Error Analysis 447
    - A.4.1 Rules for Estimating Errors 448
- Appendix B
- Physical Principles** 451
- Appendix C
- Mechanics of Materials** 456
- C.1 Stress and Strain Relations 456
- Index** 461