

Practical RF System Design



William F. Egan

CONTENTS

PREFACE	xvii
GETTING FILES FROM THE WILEY ftp AND INTERNET SITES	xix
SYMBOLS LIST AND GLOSSARY	xxi
1 INTRODUCTION	1
1.1 System Design Process / 1	
1.2 Organization of the Book / 2	
1.3 Appendixes / 3	
1.4 Spreadsheets / 3	
1.5 Test and Simulation / 3	
1.6 Practical Skepticism / 4	
1.7 References / 5	
2 GAIN	7
2.1 Simple Cases / 8	
2.2 General Case / 9	
2.2.1 <i>S</i> Parameters / 9	
2.2.2 Normalized Waves / 11	
2.2.3 <i>T</i> Parameters / 12	

2.2.4	Relationships Between S and T Parameters	/ 13
2.2.5	Restrictions on T Parameters	/ 14
2.2.6	Cascade Response	/ 14
2.3	Simplification: Unilateral Modules	/ 15
2.3.1	Module Gain	/ 15
2.3.2	Transmission Line Interconnections	/ 16
2.3.3	Overall Response, Standard Cascade	/ 25
2.3.4	Combined with Bilateral Modules	/ 28
2.3.5	Lossy Interconnections	/ 32
2.3.6	Additional Considerations	/ 38
2.4	Nonstandard Impedances	/ 40
2.5	Use of Sensitivities to Find Variations	/ 40
2.6	Summary	/ 43
	Endnotes	/ 45

3 NOISE FIGURE

47

3.1	Noise Factor and Noise Figure	/ 47
3.2	Modules in Cascade	/ 49
3.3	Applicable Gains and Noise Factors	/ 54
3.4	Noise Figure of an Attenuator	/ 55
3.5	Noise Figure of an Interconnect	/ 56
3.6	Cascade Noise Figure	/ 56
3.7	Expected Value and Variance of Noise Figure	/ 58
3.8	Impedance-Dependent Noise Factors	/ 59
3.8.1	Representation	/ 60
3.8.2	Constant-Noise Circles	/ 61
3.8.3	Relation to Standard Noise Factor	/ 62
3.8.4	Using the Theoretical Noise Factor	/ 64
3.8.5	Summary	/ 65
3.9	Image Noise, Mixers	/ 65
3.9.1	Effective Noise Figure of the Mixer	/ 66
3.9.2	Verification for Simple Cases	/ 69
3.9.3	Examples of Image Noise	/ 69
3.10	Extreme Mismatch, Voltage Amplifiers	/ 74
3.10.1	Module Noise Factor	/ 76
3.10.2	Cascade Noise Factor	/ 78
3.10.3	Combined with Unilateral Modules	/ 79
3.10.4	Equivalent Noise Factor	/ 79

- 3.11 Using Noise Figure Sensitivities / 79
- 3.12 Mixed Cascade Example / 80
 - 3.12.1 Effects of Some Resistor Changes / 81
 - 3.12.2 Accounting for Other Reflections / 82
 - 3.12.3 Using Sensitivities / 82
- 3.13 Gain Controls / 84
 - 3.13.1 Automatic Gain Control / 84
 - 3.13.2 Level Control / 86
- 3.14 Summary / 88
 - Endnotes / 90

4 NONLINEARITY IN THE SIGNAL PATH

91

- 4.1 Representing Nonlinear Responses / 91
- 4.2 Second-Order Terms / 92
 - 4.2.1 Intercept Points / 93
 - 4.2.2 Mathematical Representations / 95
 - 4.2.3 Other Even-Order Terms / 97
- 4.3 Third-Order Terms / 97
 - 4.3.1 Intercept Points / 99
 - 4.3.2 Mathematical Representations / 100
 - 4.3.3 Other Odd-Order Terms / 101
- 4.4 Frequency Dependence and Relationship Between Products / 102
- 4.5 Nonlinear Products in the Cascades / 103
 - 4.5.1 Two-Module Cascade / 104
 - 4.5.2 General Cascade / 105
 - 4.5.3 IMs Adding Coherently / 106
 - 4.5.4 IMs Adding Randomly / 108
 - 4.5.5 IMs That Do Not Add / 109
 - 4.5.6 Effect of Mismatch on IPs / 110
- 4.6 Examples: Spreadsheets for IMs in a Cascade / 111
- 4.7 Anomalous IMs / 115
- 4.8 Measuring IMs / 116
- 4.9 Compression in the Cascade / 119
- 4.10 Other Nonideal Effects / 121
- 4.11 Summary / 121
 - Endnote / 122

- 5.1 Intermodulation of Noise / 123
 - 5.1.1 Preview / 124
 - 5.1.2 Flat Bandpass Noise / 125
 - 5.1.3 Second-Order Products / 125
 - 5.1.4 Third-Order Products / 130
- 5.2 Composite Distortion / 133
 - 5.2.1 Second-Order IMs (CSO) / 134
 - 5.2.2 Third-Order IMs (CTB) / 136
 - 5.2.3 CSO and CTB Example / 136
- 5.3 Dynamic Range / 137
 - 5.3.1 Spurious-Free Dynamic Range / 137
 - 5.3.2 Other Range Limitations / 139
- 5.4 Optimizing Cascades / 139
 - 5.4.1 Combining Parameters on One Spreadsheet / 139
 - 5.4.2 Optimization Example / 143
- 5.5 Spreadsheet Enhancements / 146
 - 5.5.1 Lookup Tables / 146
 - 5.5.2 Using Controls / 147
- 5.6 Summary / 147
 - Endnotes / 147

6 ARCHITECTURES THAT IMPROVE LINEARITY

- 6.1 Parallel Combining / 149
 - 6.1.1 90° Hybrid / 150
 - 6.1.2 180° Hybrid / 152
 - 6.1.3 Simple Push-Pull / 154
 - 6.1.4 Gain / 155
 - 6.1.5 Noise Figure / 156
 - 6.1.6 Combiner Trees / 156
 - 6.1.7 Cascade Analysis of a Combiner Tree / 157
- 6.2 Feedback / 158
- 6.3 Feedforward / 159
 - 6.3.1 Intermods and Harmonics / 160
 - 6.3.2 Bandwidth / 161
 - 6.3.3 Noise Figure / 161
- 6.4 Nonideal Performance / 162
- 6.5 Summary / 163
 - Endnotes / 163

- 7.1 Basics / 165
 - 7.1.1 The Mixer / 165
 - 7.1.2 Conversion in Receivers / 167
 - 7.1.3 Spurs / 168
 - 7.1.4 Conversion in Synthesizers and Exciters / 170
 - 7.1.5 Calculators / 170
 - 7.1.6 Design Methods / 170
 - 7.1.7 Example / 171
- 7.2 Spurious Levels / 171
 - 7.2.1 Dependence on Signal Strength / 171
 - 7.2.2 Estimating Levels / 173
 - 7.2.3 Strategy for Using Levels / 175
- 7.3 Two-Signal IMs / 176
- 7.4 Power Range for Predictable Levels / 177
- 7.5 Spur Plot, LO Reference / 180
 - 7.5.1 Spreadsheet Plot Description / 180
 - 7.5.2 Example of a Band Conversion / 182
 - 7.5.3 Other Information on the Plot / 184
- 7.6 Spur Plot, IF Reference / 186
- 7.7 Shape Factors / 196
 - 7.7.1 Definitions / 197
 - 7.7.2 RF Filter Requirements / 197
 - 7.7.3 IF Filter Requirements / 200
- 7.8 Double Conversion / 202
- 7.9 Operating Regions / 203
 - 7.9.1 Advantageous Regions / 203
 - 7.9.2 Limitation on Downconversion, Two-by-Twos / 206
 - 7.9.3 Higher Values of m / 209
- 7.10 Examples / 211
- 7.11 Note on Spur Plots Used in This Chapter / 216
- 7.12 Summary / 216
 - Endnotes / 217

8 CONTAMINATING SIGNALS IN SEVERE NONLINEARITIES

- 8.1 Decomposition / 220
- 8.2 Hard Limiting / 223
- 8.3 Soft Limiting / 223

- 8.4 Mixers, Through the LO Port / 225
 - 8.4.1 AM Suppression / 225
 - 8.4.2 FM Transfer / 226
 - 8.4.3 Single-Sideband Transfer / 226
 - 8.4.4 Mixing Between LO Components / 228
 - 8.4.5 Troublesome Frequency Ranges in the LO / 228
 - 8.4.6 Summary of Ranges / 235
 - 8.4.7 Effect on Noise Figure / 236
- 8.5 Frequency Dividers / 240
 - 8.5.1 Sideband Reduction / 240
 - 8.5.2 Sampling / 241
 - 8.5.3 Internal Noise / 242
- 8.6 Frequency Multipliers / 242
- 8.7 Summary / 243
- Endnotes / 244

9 PHASE NOISE

245

- 9.1 Describing Phase Noise / 245
- 9.2 Adverse Effects of Phase Noise / 247
 - 9.2.1 Data Errors / 247
 - 9.2.2 Jitter / 248
 - 9.2.3 Receiver Desensitization / 249
- 9.3 Sources of Phase Noise / 250
 - 9.3.1 Oscillator Phase Noise Spectrums / 250
 - 9.3.2 Integration Limits / 252
 - 9.3.3 Relationship Between Oscillator S_{ϕ} and L_{ϕ} / 252
- 9.4 Processing Phase Noise in a Cascade / 252
 - 9.4.1 Filtering by Phase-Locked Loops / 253
 - 9.4.2 Filtering by Ordinary Filters / 254
 - 9.4.3 Implication of Noise Figure / 255
 - 9.4.4 Transfer from Local Oscillators / 255
 - 9.4.5 Transfer from Data Clocks / 256
 - 9.4.6 Integration of Phase Noise / 258
- 9.5 Determining the Effect on Data / 258
 - 9.5.1 Error Probability / 258
 - 9.5.2 Computing Phase Variance, Limits of Integration / 259
 - 9.5.3 Effect of the Carrier-Recovery Loop on Phase Noise / 260

9.5.4	Effect of the Loop on Additive Noise / 262
9.5.5	Contribution of Phase Noise to Data Errors / 263
9.5.6	Effects of the Low-Frequency Phase Noise / 268
9.6	Other Measures of Phase Noise / 269
9.6.1	Jitter / 269
9.6.2	Allan Variance / 271
9.7	Summary / 271
	Endnote / 272

APPENDIX A OP AMP NOISE FACTOR CALCULATIONS 273

A.1	Invariance When Input Resistor Is Redistributed / 273
A.2	Effect of Change in Source Resistances / 274
A.3	Model / 276

APPENDIX B REPRESENTATIONS OF FREQUENCY BANDS, IF NORMALIZATION 279

B.1	Passbands / 279
B.2	Acceptance Bands / 279
B.3	Filter Asymmetry / 286

APPENDIX C CONVERSION ARITHMETIC 289

C.1	Receiver Calculator / 289
C.2	Synthesis Calculator / 291

APPENDIX E EXAMPLE OF FREQUENCY CONVERSION 293

APPENDIX F SOME RELEVANT FORMULAS 303

F.1	Decibels / 303
F.2	Reflection Coefficient and SWR / 304
F.3	Combining SWRs / 306
F.3.1	Summary of Results / 306
F.3.2	Development / 307
F.3.3	Maximum SWR / 308
F.3.4	Minimum SWR / 309
F.3.5	Relaxing Restrictions / 309
F.4	Impedance Transformations in Cables / 310
F.5	Smith Chart / 310

APPENDIX G	TYPES OF POWER GAIN	313
G.1	Available Gain / 313	
G.2	Maximum Available Gain / 313	
G.3	Transducer Gain / 314	
G.4	Insertion Gain / 315	
G.5	Actual Gain / 315	
APPENDIX H	FORMULAS RELATING TO IMs AND HARMONICS	317
H.1	Second Harmonics / 317	
H.2	Second-Order IMs / 318	
H.3	Third Harmonics / 318	
H.4	Third-Order IMs / 319	
H.5	Definitions of Terms / 320	
APPENDIX I	CHANGING THE STANDARD IMPEDANCE	321
I.1	General Case / 321	
I.2	Unilateral Module / 323	
APPENDIX L	POWER DELIVERED TO THE LOAD	325
APPENDIX M	MATRIX MULTIPLICATION	327
APPENDIX N	NOISE FACTORS — STANDARD AND THEORETICAL	329
N.1	Theoretical Noise Factor / 329	
N.2	Standard Noise Factor / 331	
N.3	Standard Modules and Standard Noise Factor / 332	
N.4	Module Noise Factor in a Standard Cascade / 333	
N.5	How Can This Be? / 334	
N.6	Noise Factor of an Interconnect / 334	
N.6.1	Noise Factor with Mismatch / 335	
N.6.2	In More Usable Terms / 336	
N.6.3	Verification / 338	
N.6.4	Comparison with Theoretical Value / 340	
N.7	Effect of Source Impedance / 341	
N.8	Ratio of Power Gains / 342	
	Endnote / 343	

APPENDIX P	IM PRODUCTS IN MIXERS	345
APPENDIX S	COMPOSITE S PARAMETERS	349
APPENDIX T	THIRD-ORDER TERMS AT INPUT FREQUENCY	353
APPENDIX V	SENSITIVITIES AND VARIANCE OF NOISE FIGURE	355
APPENDIX X	CROSSOVER SPURS	359
APPENDIX Z	NONSTANDARD MODULES	363
Z.1	Gain of Cascade of Modules Relative to Tested Gain /	363
Z.2	Finding Maximum Available Gain of a Module /	366
Z.3	Interconnects /	367
Z.4	Equivalent <i>S</i> Parameters /	367
Z.5	<i>S</i> Parameters for Cascade of Nonstandard Modules /	368
	Endnote /	369
REFERENCES		371
	Endnote /	377
INDEX		379