

Programmable Logic Controllers

Programming Methods and Applications

John R. Hackworth
Frederick D. Hackworth, Jr.



Contents

CHAPTER 1 LADDER DIAGRAM FUNDAMENTALS 1

Objectives	1
Introduction	1
1-1 Basic Components and Their Symbols	2
1-2 Fundamentals of Ladder Diagrams	13
1-3 Machine Control Terminology	31
Summary	33

CHAPTER 2 THE PROGRAMMABLE LOGIC CONTROLLER 35

Objectives	35
Introduction	35
2-1 A Brief History	36
2-2 PLC Configurations	37
2-3 System Block Diagram	42
2-4 Update-Solve the Ladder-Update	43
2-5 Update	44
2-6 Solve the Ladder	45
Summary	48

CHAPTER 3 FUNDAMENTAL PLC PROGRAMMING 50

Objectives	50
Introduction	50
3-1 Physical Components vs. Program Components	51
3-2 Example Problem—Lighting Control	56
3-3 Internal Relays	58
3-4 Disagreement Circuit	59

3-5	Majority Circuit	59
3-6	Oscillator	62
3-7	Holding (also called Sealed, or Latched) Contacts	64
3-8	Always-ON and Always-OFF Contacts	65
3-9	Ladder Diagrams Having More Than One Rung	67
	Summary	69

CHAPTER 4 ADVANCED PROGRAMMING TECHNIQUES 72

	Objectives	72
	Introduction	72
4-1	Ladder Program Execution Sequence	73
4-2	Flip Flops	73
4-3	R-S Flip Flop	73
4-4	One Shot	74
4-5	D Flip Flop	77
4-6	T Flip Flop	79
4-7	J-K Flip Flop	81
4-8	Counters	83
4-9	Sequencers	85
4-10	Timers	87
4-11	Master Control Relays and Control Zones	96
	Summary	98

CHAPTER 5 MNEMONIC PROGRAMMING CODE 103

	Objectives	103
	Introduction	103
5-1	AND Ladder Rung	104
5-2	Entering Normally Closed Contacts	105
5-3	OR Ladder Rung	106
5-4	Simple Branches	107
5-5	Complex Branches	110
	Summary	112

CHAPTER 6 WIRING TECHNIQUES 115

	Objectives	115
	Introduction	115
6-1	PLC Power Connection	116

6-2	Input Wiring	119
6-3	Inputs Having a Single Common	121
6-4	Isolated Inputs	124
6-5	Output Wiring	126
6-6	Relay Outputs	127
6-7	Solid State Outputs	131
	Summary	137

CHAPTER 7 ANALOG I/O 139

	Objectives	139
	Introduction	139
7-1	Analog (A/D) Input	110
7-2	Analog (D/A) Output	144
7-3	Analog Data Handling	145
7-4	Analog Input Potential Problems	146
	Summary	147

CHAPTER 8 DISCRETE POSITION SENSORS 150

	Objectives	150
	Introduction	150
8-1	Sensor Output Classification	151
8-2	Connecting Discrete Sensors to PLC Inputs	154
8-3	Proximity Sensors	156
8-4	Inductive Proximity Sensors	156
8-5	Capacitive Proximity Sensors	159
8-6	Ultrasonic Proximity Sensors	161
8-7	Optical Proximity Sensors	163
	Summary	167

CHAPTER 9 ENCODERS, TRANSDUCERS, AND ADVANCED SENSORS 169

	Objectives	169
	Introduction	169
9-1	Temperature	170
9-2	Liquid Level	175
9-3	Force	177
9-4	Pressure/Vacuum	181
9-5	Flow	186

9-6	Inclination	192
9-7	Acceleration	193
9-8	Angle Position Sensors	194
9-9	Linear Displacement	204
	Summary	209

CHAPTER 10 CLOSED-LOOP AND PID CONTROL 212

	Objectives	212
	Introduction	212
10-1	Simple Closed-Loop Systems	212
10-2	Problems with Simple Closed-Loop Systems	214
10-3	Closed-Loop Systems Using Proportional, Integral, Derivative (PID)	218
10-4	Derivative Function	220
10-5	Integral Function	225
10-6	The PID in Programmable Logic Controllers	228
10-7	Tuning the PID	229
10-8	The "Adjust and Observe" Tuning Method	231
10-9	The Ziegler-Nichols Tuning Method	233
10-10	Autotuning PID Systems	239
	Summary	240

CHAPTER 11 MOTOR CONTROLS 242

	Objectives	242
	Introduction	242
11-1	AC Motor Starter	243
11-2	AC Motor Overload Protection	245
11-3	Specifying a Motor Starter	247
11-4	DC Motor Controller	248
11-5	Variable Speed (Variable Frequency) AC Motor Drive	255
	Summary	258

CHAPTER 12 SYSTEM INTEGRITY AND SAFETY 260

Objectives 260

Introduction 260

12-1 System Integrity 260

12-2 Equipment Temperature Considerations 263

12-3 Fail Safe Wiring and Programming 264

12-4 Safety Interlocks 268

Summary 272

APPENDIX A LOGIC SYMBOLS 274

APPENDIX B INDUSTRIAL ELECTRICAL SYMBOLS 276

BIBLIOGRAPHY 281

GLOSSARY 283

INDEX 297