

Practical Interfacing in the Laboratory

Using a PC for instrumentation, data analysis, and control

Stephen E. Derenzo

CAMBRIDGE

Contents

Preface

xiii

Acknowledgments

xvii

1 Digital tools 1

| | | |
|------|--|----|
| 1.1 | Introduction | 1 |
| 1.2 | The microcomputer | 2 |
| 1.3 | Number systems | 5 |
| 1.4 | Digital building blocks | 8 |
| 1.5 | Digital counters/timers | 13 |
| 1.6 | Parallel and serial input/output ports | 18 |
| 1.7 | Digital data-acquisition procedures | 29 |
| 1.8 | Switch debouncing | 33 |
| 1.9 | Digital interfacing standards | 35 |
| 1.10 | Problems | 44 |
| 1.11 | Additional reading | 51 |

Laboratory exercises

| | | |
|----|--|----|
| 1. | Introduction to C programming | 53 |
| 2. | Measuring event times | 58 |
| 3. | Digital interfacing: switches and lights | 66 |

2 Analog tools 75

| | | |
|-----|--|----|
| 2.1 | Introduction | 75 |
| 2.2 | Operational-amplifier circuits | 76 |
| 2.3 | Op-amp characteristics | 85 |
| 2.4 | Instrumentation and isolation amplifiers | 89 |

| | | |
|-----|---------------------|-----|
| 2.5 | Noise sources | 94 |
| 2.6 | Analog filtering | 98 |
| 2.7 | The power amplifier | 117 |
| 2.8 | Problems | 118 |
| 2.9 | Additional reading | 127 |

Laboratory exercises

| | | |
|----|--------------------------------|-----|
| 4. | Operational-amplifier circuits | 128 |
| 5. | Instrumentation amplifiers | 136 |
| 6. | Analog filtering | 145 |

3 Analog ↔ digital conversion and sampling

| | | |
|-----|--------------------------------------|-----|
| 3.1 | Introduction | 153 |
| 3.2 | Digital-to-analog converter circuits | 153 |
| 3.3 | Analog-to-digital converter circuits | 161 |
| 3.4 | The sample-and-hold amplifier | 173 |
| 3.5 | Sampling analog waveforms | 180 |
| 3.6 | Frequency aliasing | 183 |
| 3.7 | Available data-acquisition systems | 186 |
| 3.8 | Problems | 187 |
| 3.9 | Additional reading | 200 |

Laboratory exercises

| | | |
|-----|--|-----|
| 7. | Introduction to A/D and D/A conversion | 201 |
| 8. | D/A conversion and waveform generation | 206 |
| 9. | A/D conversion and periodic sampling | 213 |
| 10. | Frequency aliasing | 221 |

4 Sensors and actuators

| | | |
|-----|--------------------------------|-----|
| 4.1 | Introduction | 226 |
| 4.2 | Position and angle sensors | 228 |
| 4.3 | Temperature transducers | 234 |
| 4.4 | Strain-sensing elements | 253 |
| 4.5 | Force and pressure transducers | 255 |
| 4.6 | Measuring light | 261 |
| 4.7 | Producing visible light | 268 |

| | |
|---|-----|
| 4.8 Ionic potentials | 271 |
| 4.9 The detection and measurement of ionizing radiation | 274 |
| 4.10 Measuring time | 277 |
| 4.11 Problems | 278 |
| 4.12 Additional reading | 298 |

Laboratory exercises

| | |
|---------------------------------------|-----|
| 11. Measuring angular position | 300 |
| 12. Measuring temperature | 305 |
| 13. Measuring strain and force | 311 |
| 14. Measuring light with a photodiode | 316 |
| 15. The thermoelectric heat pump | 322 |
| 16. Electrodes and ionic media | 329 |
| 17. The human heart | 334 |
| 18. The electromyogram (EMG) | 343 |
| 19. The electrooculogram (EOG) | 352 |

5 Data analysis and control 360

| | |
|-------------------------------------|-----|
| 5.1 Introduction | 360 |
| 5.2 The Gaussian-error distribution | 360 |
| 5.3 Student's <i>t</i> test | 366 |
| 5.4 Least-squares fitting | 372 |
| 5.5 The chi-squared statistic | 375 |
| 5.6 Solving nonlinear equations | 379 |
| 5.7 Monte Carlo simulation | 383 |
| 5.8 Fourier transforms | 385 |
| 5.9 Digital filters | 415 |
| 5.10 Control techniques | 419 |
| 5.11 Problems | 427 |
| 5.12 Additional reading | 448 |

Laboratory exercises

| | |
|--|-----|
| 20. Analog ↔ digital conversion and least-squares fitting | 449 |
| 21. Fast Fourier transforms of sampled data | 454 |
| 22. Fast Fourier transforms of the human voice | 461 |
| 23. Digital filtering | 471 |
| 24. Process compensation using Fourier deconvolution and digital filtering | 477 |
| 25. Analog temperature control using a resistive heater | 485 |

| | |
|---|-----|
| 26. Temperature control using the computer and a resistive heater | 490 |
| 27. Temperature control using the computer and a thermoelectric heat pump | 497 |
| Appendix A Grounding and shielding | 504 |
| A.1 Introduction | 504 |
| A.2 Interference noise due to common impedance | 504 |
| A.3 Interference noise due to capacitive coupling | 505 |
| A.4 General rules to follow | 506 |
| Appendix B Experimental uncertainties | 508 |
| B.1 Multimeter accuracy | 508 |
| B.2 Propagation of random error | 508 |
| Appendix C C programming tips | 510 |
| C.1 Declare all variables | 510 |
| C.2 Arithmetic statements | 510 |
| C.3 Conditional tests | 511 |
| C.4 Conditional operators | 511 |
| C.5 Indexed looping | 511 |
| C.6 Bitwise logical operators | 512 |
| C.7 Increment and decrement operators | 512 |
| C.8 The printf statement | 513 |
| C.9 Defining your own functions | 513 |
| C.10 “Including” your own functions | 514 |
| C.11 Opening and writing to files of arbitrary name | 515 |
| C.12 Using library functions | 515 |
| C.13 Allocating large storage arrays | 516 |
| C.14 General format rules for C programs | 516 |
| Appendix D Numerical methods and C functions | 517 |
| D.1 Introduction | 517 |
| D.2 Fast Fourier transform | 517 |
| D.3 Minimization function PARFIT | 520 |
| D.4 The uncertainty estimation function VARFIT | 529 |
| D.5 Numerical evaluation of functions defined by integrals | 542 |
| D.6 Function inversion using Newton’s method | 549 |
| D.7 Function inversion using quadratic approximation | 549 |
| D.8 Random number generator | 550 |
| Appendix E Summary of Data Translation DT3010 PCI plug-in card | 553 |
| E.1 Introduction | 553 |
| E.2 Parallel output | 553 |
| E.3 Parallel input | 556 |

| | |
|--|-----|
| E.4 Analog output | 556 |
| E.5 Analog input | 557 |
| E.6 Using the DT3010 board with the Microsoft visual C++ compiler | 557 |
| Appendix F Using the digital oscilloscope to record waveforms | 558 |
| F.1 Introduction | 558 |
| F.2 Capturing the waveform | 558 |
| F.3 Printing the waveform | 558 |
| Appendix G Electrical hazards and safety | 560 |
| G.1 Introduction | 560 |
| G.2 Electrical power | 561 |
| G.3 The ground fault interrupter circuit | 563 |
| G.4 The isolation transformer | 564 |
| G.5 Typical accident scenarios | 564 |
| G.6 Methods of accident prevention | 564 |
| Appendix H Standard resistor and capacitor values | 566 |
| H.1 Standard resistor values and color codes | 566 |
| H.2 Standard capacitor values and codes | 566 |
| Appendix I ASCII character codes | 569 |
| I.1 ASCII character set codes | 569 |
| <i>Glossary</i> | 572 |
| <i>Index</i> | 602 |